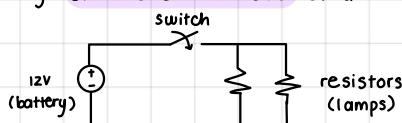




chapter 1

INTRODUCTION

- main purpose of electrical engineering systems are transferring energy from one place to another, communicating info, & processing info for better presentation & analysis
- e.g. electric circuit model of a headlights system



- ↳ battery converts chemical into electrical energy that forces electrons to flow around circuit & transfer energy
- ↳ wires made from conducting material (e.g. copper)
- ↳ switch controls operation of system
 - ↳ closed means electric current (moving charges) can flow through circuit
- ↳ resistors convert electric energy into heat & light

ELECTRIC CURRENT

- when electric charges move through element / wire in circuit, create electric current (denoted by i)
 - ↳ dir of current, is dir of movement of +ve charges
 - for moving -ve charges, dir of i is opposite dir
 - current $i(t)$ is defined as time ROC of charge $q(t)$: $i(t) = \frac{dq(t)}{dt}$
 - ↳ current $i(t)$ is measured in Amperes (A)
 - ↳ charge $q(t)$ is in Coulombs (C)
 - ↳ time t is in seconds (s)
- charge in terms of current : $q(t) = \int_{t_0}^t i(T) dT + q(t_0)$
 - ↳ t_0 is usually given
 - ↳ T is dummy variable
- acc dir of currents for elements in circuit are usually unknown before analysing
 - value of current for same element can be +ve & -ve at diff times
- reference dirs are assigned arbitrarily to elements before analyzing
 - if value of current is +ve, then acc dir is same as reference
- in circuit analysis, currents are classified based on how current changes w/time.
 - ↳ direct current (DC): current flows in one dir
 - e.g. constant current $i = 3A$
 - ↳ alternating current (AC): current reverses dir
 - e.g. sinusoidal current $i(t) = 2\sin(5t)$
 - ↳ Time varying: any other type of current
 - e.g. $i(t) = e^{-t}$

ELECTRIC VOLTAGE

- motion of charge (current) in circuit is created by force called electromotive force (emf), potential diff, or electric voltage
- electric voltage is amount of energy required to move unit charge from one point to another
 - ↳ moving charges transfer energy from one point to another
 - ↳ $V = \frac{dw}{dq}$
 - w is energy measured in joules (J)

- q is charge in coulombs (C)
- v is voltage in volts ($1 \text{ V} = 1 \text{ J/C}$)
- when charges move through element, voltage diff is established across it since energy is absorbed/supplied
 - ↳ polarities (+ i -) are used to distinguish higher (+) from lower (-) potential
- actual polarities of voltages for elements are usually unknown so reference polarities are assigned arbitrarily
- voltages are classified similarly to currents
 - ↳ constant over time is DC voltage
 - e.g. $v = 2V$
 - ↳ reverses over time is AC voltage
 - e.g. $v = 3\cos(2t)$

POWER AND ENERGY

- power is time ROC of energy : $p = \frac{dw}{dt}$
 - ↳ w is in joules (J)
 - ↳ p is in watts (W)
- above equation is rarely used since:


$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt}$$

$$p = v \cdot i$$
- ↳ power is product of voltage & current

NOTE

$$\cdot E = \int_{t_0}^t p(t) dt \quad \ddagger$$

$1 \text{ J} = 1 \text{ Ws}$

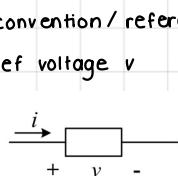

- ↳ ref absorbed power is $p_{abs} = v \cdot i$
 - if $p_{abs} > 0$, power is actually absorbed
 - if $p_{abs} < 0$, power is actually supplied
- ↳ aka passive sign convention (PSC)

NOTE

- if p_{abs} doesn't comply w/PSC (i.e. current goes from -ve to +ve sign of voltage), then

$$p_{abs} = -v \cdot i$$

- convention/reference for element to supply / deliver power is when dir of ref current i is from -ve to +ve sign of ref voltage v
 - ↳ ref supplied power is $p_{sup} = v \cdot i$
 - if $p_{sup} > 0$, power is actually supplied
 - if $p_{sup} < 0$, power is actually absorbed
 - ↳ if p_{sup} is computed for element that complies w/PSC, then $p_{sup} = -v \cdot i$
 - ↳ for every element, $p_{abs} = -p_{sup}$

- for every circuit, Principle of Conservation of Power / Energy states that

$$\sum \text{absorbed powers} = \sum \text{supplied powers}$$

- ↳ i.e. algebraic sum of all powers in circuit is 0 : $\sum p_n = 0$
- to compute energy from power, use $p = \frac{dw}{dt}$:

$$dw = p dt$$

$$w(t) = \int_{-\infty}^t p(\tau) d\tau$$

$$= \int_{-\infty}^t v(\tau) i(\tau) d\tau$$

- ↳ energy from time t_1 to t_2 is $w = w(t_2) - w(t_1)$

$$w = \int_{t_1}^{t_2} p(\tau) d\tau$$


CIRCUIT ELEMENTS

- ideal circuit elements are used to model real physical components in electric circuit
- classified as active / passive elements
 - active elements generate / supply power / energy to rest of circuit
 - e.g. voltage source & current source
 - sub-classified into independent / dependent sources
 - passive elements can't supply power / energy
 - e.g. resistors absorb energy
 - e.g. capacitors & inductors store & later release energy
- circuit elements are also classified as linear / nonlinear elements
 - linear element has voltage & current in linear relation (e.g. $v = 5i$)

ideal independent voltage source has specified voltage across its terminals independent of current & other elements

↳ physical sources like batteries & generators can be apx by these


↳ 2 common symbols:

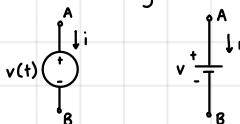

ideal independent current source has specified current independent of voltage & other elements

↳ good apx is electronic amplifier

↳ common symbol:

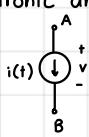


since models are ideal, they don't exist as separate physical elements


↳ combine w/ other models to more accurately rep real elements

↳ e.g. real physical battery modeled by ideal constant voltage source w/ resistor

short circuit: voltage btwn 2 nodes is 0

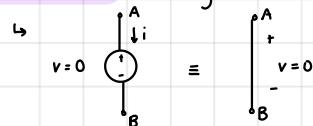


open circuit: current btwn 2 nodes is 0

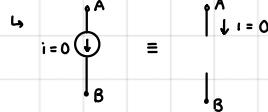


series connection: 2 elements connected in series if they're only 2 elements connected to node

↳ have same current

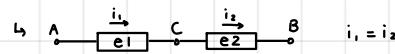


parallel connection: 2+ elements connected in parallel if connected btwn same 2 nodes

↳ have same voltage

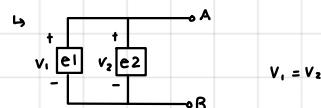


series connection of ideal voltage sources is always valid while of current sources is not valid b/c in general,

$i_1 \neq i_2$

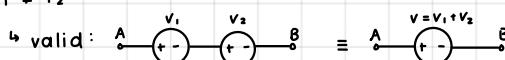


↳ not valid:

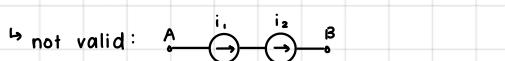


parallel connection of ideal current sources is always valid while of voltage sources is not valid b/c in general,

$$V_1 \neq V_2$$

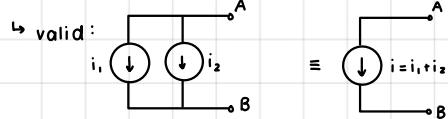

↳ not valid:

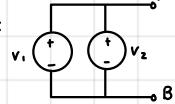

electronic devices (e.g. transistor or amplifier) are modeled by dependent voltage/current sources


also called controlled sources

↳ dependent voltage/current sources can be controlled by voltage/current in another circuit element


↳ use diamond shape

↳ 4 models:

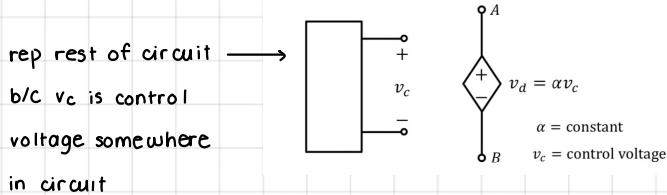
° voltage-controlled voltage source (VCVS)



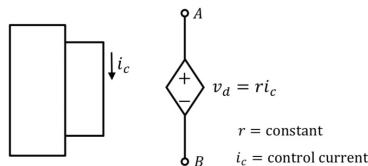
° current-controlled voltage source (CCVS)



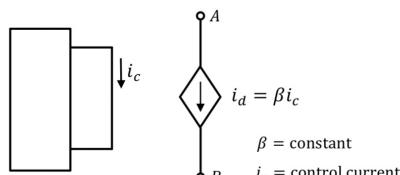° current-controlled current source (CCCS)



° voltage-controlled current source (VCCS)

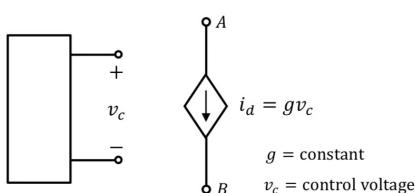

chapter 2

RESISTORS AND OHM'S LAW

- flow of current through physical element encounters resistance, denoted by R
 - ↳ results in voltage drop
 - ↳ converts electrical energy to heat
- ideal circuit element is resistor



- Ohm's Law: voltage across resistor is proportional to current by a constant of R
 - ↳ $v = Ri$
 - R is tve constant & measured in ohms (Ω)
 - $1 \Omega = \frac{1V}{1A}$
 - ↳ if resistor doesn't comply w/ PSC, Ohm's law is $v = -Ri$
 - ↳ when $R = 0$, resistor is short circuit
 - ↳ when $R \rightarrow \infty$, resistor is open circuit
- power absorbed by resistor is $p = vi = Ri^2 = \frac{v^2}{R}$
 - ↳ since $R \geq 0$, then resistor always absorbs power
- practical physical resistor has 2 values: resistance R & power rating p_{max}
 - ↳ in circuit, ensure each $p < p_{max}$

- conductance of resistor, denoted by G , is reciprocal of resistance

$$\hookrightarrow G = \frac{1}{R}$$

↳ unit is Siemens (S) & $1S = 1\Omega^{-1}$

- Ohm's law for conductance:


$$\hookrightarrow v = \frac{i}{G}$$

$$\hookrightarrow i = Gv$$


- power for conductance is $p = vi = \frac{i^2}{G} = Gv^2$

KIRCHHOFF'S CURRENT LAW (KCL)

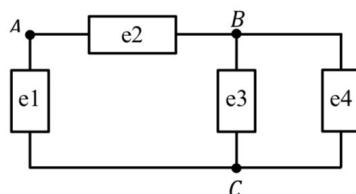- node: point/junction in circuit where 2 or more elements are connected



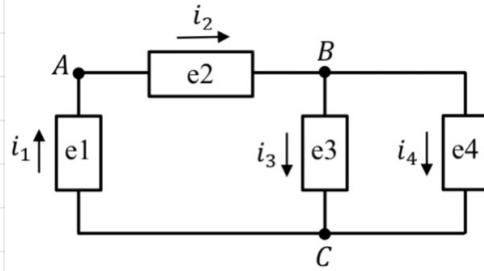- ↳ e.g. circuit above has 3 nodes
- KCL states that algebraic sum of all currents at any node is 0
 - ↳ $\sum_n i_{in} = 0$
 - ↳ algebraic means if currents entering node are +ve, then currents leaving must be -ve (or vice versa)
 - ↳ based on law of conservation of charge
 - ↳ i.e. $\sum \text{entering currents} = \sum \text{leaving currents}$
- e.g. $i_1 = 3A$ & $i_3 = 1A$; find i_2 & i_4



SOLUTION

KCL at node A: $i_1 - i_2 = 0$

$$i_2 = i_1$$

$$i_2 = 3A$$

KCL at node B: $i_2 - i_3 - i_4 = 0$

$$i_2 - i_3 = i_4$$

$$i_4 = 3 - 1$$

$$i_4 = 2A$$

↳ KCL at node C is $i_1 - i_3 - i_4 = 0$

- not independent b/c it's sum of above 2 KCLs so it's not needed

- ↳ circuit w/ N nodes has $(N-1)$ independent KCL equations

- ↳ one current variable is used for all series elements so KCL at node A isn't needed

KIRCHHOFF'S VOLTAGE LAW (KVL)

- loop: closed path in circuit in which no element is encountered more than once

- mesh: loop that doesn't enclose another loop

- KVL states that algebraic sum of all voltages around any loop is 0

↳ $\sum_n V_n = 0$

- ↳ based on law of conservation of energy

- voltage drop: move from +ve to -ve side of voltage

- voltage rise: move from -ve to +ve side of voltage

- # of independent KVL equations = # of meshes

- one voltage variable is used for all parallel elements so # of KVL equations can be reduced


- another statement of KVL is sum of voltage drops btwn 2 nodes is same, regardless of path taken

NOTE

· in every circuit, there must be at least 1 source supplying power

EQUIVALENT SERIES AND PARALLEL RESISTORS

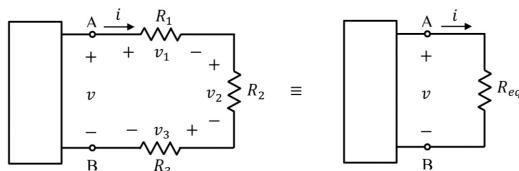- 2+ resistors connected in series have same current



↳ applying KVL & Ohm's Law: $v = v_1 + v_2 + v_3$


$$= R_1 i + R_2 i + R_3 i$$

$$= (R_1 + R_2 + R_3) i$$

$$= R_{eq} i$$

↳ $R_{eq} = R_1 + R_2 + R_3$

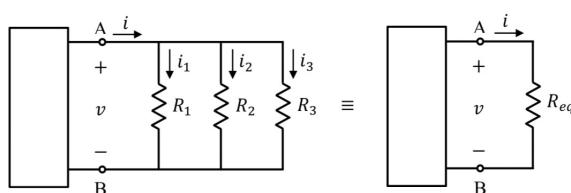- 2+ resistors connected in parallel have same voltage



↳ applying KCL & Ohm's Law: $i = i_1 + i_2 + i_3$

$$\begin{aligned} &= \frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3} \\ &= \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v \\ &= \frac{1}{R_{eq}} (v) \end{aligned}$$

↳ $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

• in terms of conductances: $G_{eq} = G_1 + G_2 + G_3$


• for special case of 2 parallel resistors: $\frac{1}{R_{eq}} = \frac{1}{R_1 + R_2}$

$$\begin{aligned} &= \frac{R_1 R_2}{R_1 + R_2} \\ &= \frac{R_1 R_2}{R_{eq}} \end{aligned}$$


$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

• for special case of short circuit in parallel w/ resistor, $R_{eq} = 0$

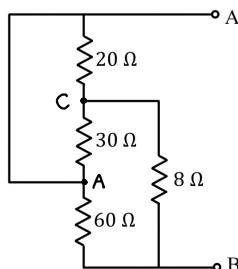• e.g. find R_{eq} btwn A & B for below circuit:



redraw circuit

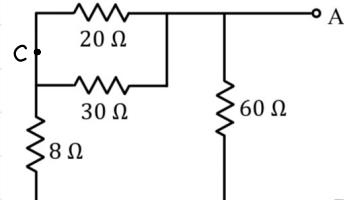


SOLUTION

$$\begin{aligned} R_{eq} &= ((20\parallel 30) + 8) \parallel 60 \\ &= \left(\frac{20 \cdot 30}{20+30} + 8 \right) \parallel 60 \\ &= (12 + 8) \parallel 60 \\ &= \frac{20 \cdot 60}{20+60} \\ &= 15 \Omega \end{aligned}$$

VOLTAGE DIVISION

sometimes, we know total voltage of 2+ resistors in series & want to know individual voltage across each resistor

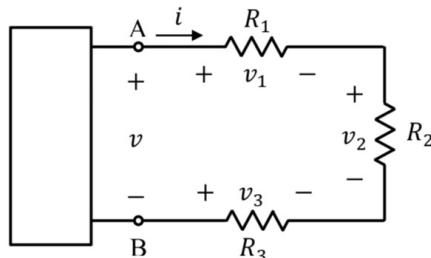↳ voltage division relations provide shortcut w/o computation of current & Ohm's Law



↳ current is $i = \frac{v}{R_1 + R_2 + R_3}$

↳ individual voltages are $v_1 = R_1 i$, $v_2 = R_2 i$, & $v_3 = -R_3 i$

↳ sub current to get voltage divider relations:

• $v_1 = \frac{R_1}{R_1 + R_2 + R_3} v$


• $v_2 = \frac{R_2}{R_1 + R_2 + R_3} v$

• $v_3 = \frac{-R_3}{R_1 + R_2 + R_3} v$

CURRENT DIVISION

sometimes, we know total current of 2+ resistors in parallel & want to know individual current through each resistor

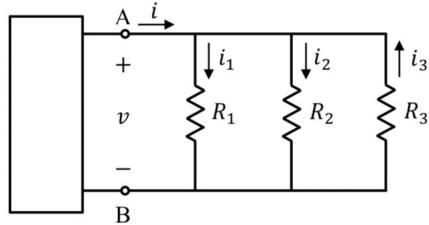↳ current division relations provide shortcut w/o computation of voltage & Ohm's Law



NOTE

more convenient to use conductance instead of resistance

↳ voltage is $v = \frac{i}{G_1 + G_2 + G_3}$

↳ individual currents are $i_1 = G_1 v$, $i_2 = G_2 v$, & $i_3 = G_3 v$

↳ sub voltage to get current divider relations

$$i_1 = \frac{G_1}{G_1 + G_2 + G_3} i$$

$$i_2 = \frac{G_2}{G_1 + G_2 + G_3} i$$

$$i_3 = \frac{G_3}{G_1 + G_2 + G_3} i$$

· for special case of 2 resistors in parallel, current divider relations can be written in terms of resistances

$$i_1 = \frac{G_1}{G_1 + G_2} i$$

$$= \frac{1/R_1 + 1/R_2}{1/R_1} i$$



$$= \frac{1}{R_1} \left(\frac{R_1 R_2}{R_1 + R_2} \right) i$$

$$i_1 = \frac{R_2}{R_1 + R_2} i$$



$$\hookrightarrow i_2 = \frac{R_1}{R_1 + R_2} i$$

SERIES AND PARALLEL CONNECTIONS OF SOURCES

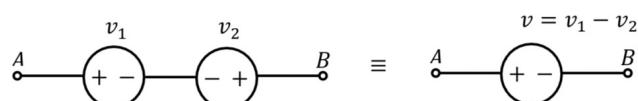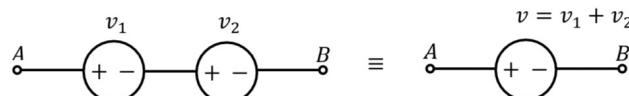· voltage sources can be connected in series but parallel connection is invalid



· current sources can be connected in parallel but series connection is invalid

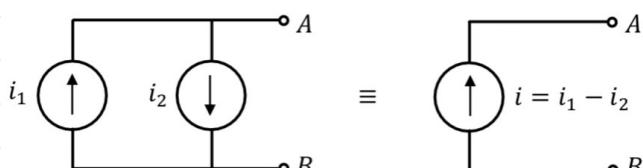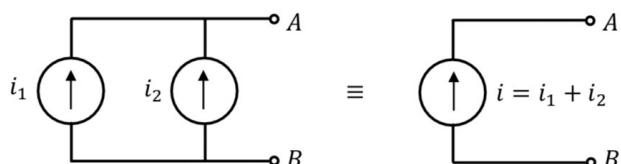

chapter 3

NODE - VOLTAGE (NODAL) ANALYSIS


- essential node: node where 3+ circuit elements are connected
- reference node: chosen arbitrarily; assumed to have zero-voltage
 - one of essential nodes
 - symbol is $\frac{1}{\square}$ or \square
 - usually chosen to have most branches
- node-voltage: voltage drop from non-ref node to ref node
- essential node-voltage: voltage drop from essential non-ref node to ref node
- procedure for nodal analysis on circuit w/ N essential nodes:

- choose ref node & label (N-1) node-voltages
- optional: assign currents to branches
- apply KCL at each non-ref essential node to get (N-1) equations
- use Ohm's Law & KVL to express currents in terms of node-voltages

↳ use 3-points rule :


$$\circ i_x = \frac{v_x}{R} = \frac{v_1 - v_2}{R}$$
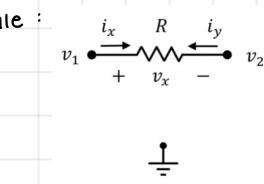
$$\circ i_y = \frac{v_x}{R} = \frac{v_2 - v_1}{R}$$



- solve resulting (N-1) linear independent equations for (N-1) unknown node-voltages

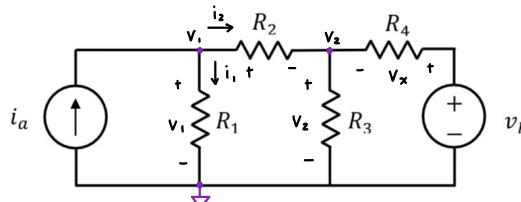- e.g. find all currents & voltages using nodal analysis



$$i_a = 3.75 \text{ A}$$

$$v_b = 6 \text{ V}$$

$$R_1 = R_3 = 2 \Omega$$

$$R_2 = R_4 = 4 \Omega$$

SOLUTION

KCL at node 1: $-i_a + i_1 + i_2 = 0$

$$\frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} = i_a$$

$$v_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - v_2 \left(\frac{1}{R_2} \right) = i_a$$

$$v_1 \left(\frac{1}{2} + \frac{1}{4} \right) - v_2 \left(\frac{1}{4} \right) = 3.75$$

$$0.75v_1 - 0.25v_2 = 3.75 \quad (1)$$

KCL at node 2: $\frac{v_2 - v_1}{R_2} + \frac{v_2}{R_3} + \frac{v_2 - v_b}{R_4} = 0$

$$v_1 \left(-\frac{1}{R_2} \right) + v_2 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) - v_b \left(\frac{1}{R_4} \right) = 0$$

$$v_1 \left(-\frac{1}{4} \right) + v_2 \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{4} \right) = \frac{6}{4}$$

$$v_2 - 0.25v_1 = 1.5$$

$$v_2 = 1.5 + 0.25v_1 \quad (2)$$

Sub (2) into (1):

$$0.75v_1 - 0.25v_2 = 3.75$$

$$0.75v_1 - 0.25(1.5 + 0.25v_1) = 3.75$$

$$0.75v_1 - 0.375 - 0.0625v_1 = 3.75$$

$$0.6875v_1 = 4.125$$

$$v_1 = 6 \text{ V}$$

use (2):

$$v_2 = 1.5 + 0.25v_1$$

$$= 1.5 + 0.25(6)$$

$$= 3 \text{ V}$$

Compute all other currents & voltages:

$$i_1 = \frac{v_1}{R_1} = \frac{6}{2} = 3 \text{ A}$$

$$i_2 = \frac{v_2}{R_3} = \frac{3}{4} = 0.75 \text{ A}$$

$$v_x = v_b - v_2 = 6 - 3 = 3 \text{ V}$$

algebraic sum of all currents entering/leaving any closed surface(i.e. supernode) is 0

↳ general KCL statement

NOTE


- branches are connections btwn nodes
- # of branches in circuit = # of circuit elements

NOTE

- when writing KCL equation at node, assume all currents leave node (unless indicated otherwise)
- leaving currents are +ve
- entering currents are -ve

↳ supernode: when voltage source is located btwn 2 essential non-ref nodes, treat them as one node tgt

e.g. use nodal analysis to find i_x

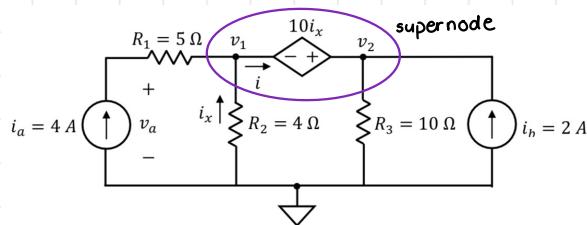

SOLUTION

$$\text{KCL at supernode: } -i_a + \frac{v_1}{R_1} + \frac{v_2}{R_3} - i_b = 0$$

$$\frac{v_1}{4} + \frac{v_2}{10} = 4 + 2$$

$$0.25v_1 + 0.1v_2 = 6 \quad (1)$$

From dependent voltage source: $10i_x = v_2 - v_1$

$$10\left(-\frac{v_1}{4}\right) = v_2 - v_1$$

$$v_2 = -\frac{5v_1}{2} + v_1$$

$$v_2 = -1.5v_1 \quad (2)$$

$$i_x = -\frac{v_1}{4}$$

$$= -\frac{60}{4}$$

$$= -15 \text{ A}$$

NOTE

R_1 has no effect on rest of circuit b/c its current is fixed by current source i_a

R_1 has effect on voltage & power for current source i_a

Sub (2) into (1):

$$0.25v_1 + 0.1(-1.5v_1) = 6$$

$$0.1v_1 = 6$$

$$v_1 = 60 \text{ V}$$

Use (2):

$$v_2 = -1.5(60)$$

$$= -90 \text{ V}$$

MESH ANALYSIS

mesh: loop that doesn't enclose another loop inside it

mesh current: imaginary current that flows around mesh w/same value & dir regardless of physical branch currents

procedure for mesh analysis on circuit w/ N meshes:


1) draw & label mesh currents

2) write KVL around each mesh; use Ohm's Law to express voltages in terms of mesh currents, using relations btwn mesh currents & branch currents

- ↳ in KVL equations, voltage-drops are +ve & voltage-rises are -ve
- ↳ when encounter resistor, assume voltage-drop in dir of movement over resistor
- ↳ assume branch current through resistor to be in dir of movement (i.e. branch current expressed directly in terms of mesh currents)

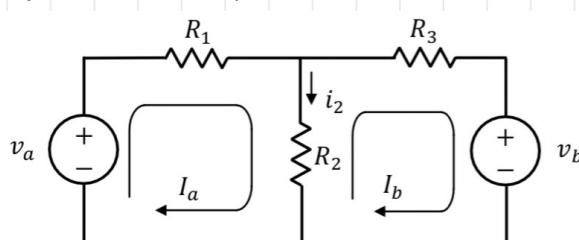3) solve resulting set of N linear equations for N unknown mesh currents

e.g. use mesh analysis to find current i_z



$$v_a = 12 \text{ V}$$

$$v_b = 3 \text{ V}$$

$$R_1 = 6 \text{ k}\Omega$$

$$R_2 = 6 \text{ k}\Omega$$

$$R_3 = 3 \text{ k}\Omega$$

SOLUTION

KVL around I_a : $-v_a + R_1 I_a + R_2 (I_a - I_b) = 0$

$$6I_a + 6(I_a - I_b) = 12$$

$$12I_a - 6I_b = 12$$

$$2I_a - I_b = 2$$

$$I_b = 2(I_a - 1) \quad (1)$$

$$\text{KVL around } I_b: R_2(I_b - I_a) + R_3 I_b + V_b = 0$$

$$6(I_b - I_a) + 3I_b = -3$$

$$9I_b - 6I_a = -3$$

$$3I_b - 2I_a = -1 \quad (2)$$

Sub (1) into (2):

$$3(2(I_a - 1)) - 2I_a = -1$$

$$I_b = 2\left(\frac{5}{4} - 1\right)$$

$$6I_a - 6 - 2I_a = -1$$

$$= 2\left(\frac{1}{4}\right)$$

$$4I_a = 5$$

$$= \frac{1}{2} \text{ mA}$$

$$I_a = \frac{5}{4} \text{ mA}$$

$$i_2 = I_a - I_b$$

$$= \frac{5}{4} - \frac{1}{2}$$


$$= \frac{3}{4} \text{ mA}$$

Thus, $i_2 = \frac{3}{4} \text{ mA}$.

supermesh: formed when 2+ meshes have common current source so they're grouped tgt to

loop doesn't pass through current source

e.g. find current i_b

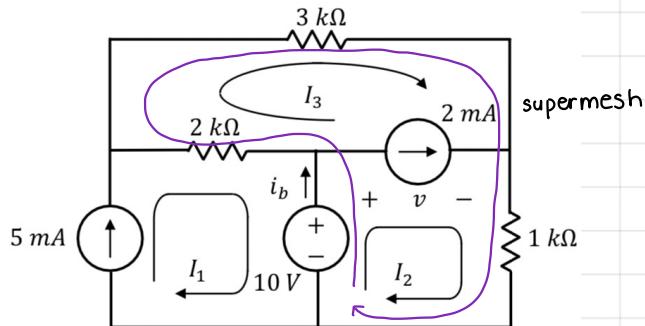

SOLUTION

$$I_1 = 5 \text{ mA}$$

$$\text{KVL around supermesh: } -10 + 2(I_3 - 5) + 3I_3 + I_2 = 0$$

$$2I_3 - 10 + 3I_3 + I_2 = 10$$

$$5I_3 + I_2 = 20 \quad (1)$$

$$\text{From current source: } 2 = I_2 - I_3$$

$$I_2 = 2 + I_3 \quad (2)$$

Sub (2) into (1):

$$5I_3 + 2 + I_3 = 20$$

$$I_2 = 2 + 3$$

$$6I_3 = 18$$

$$= 5 \text{ mA}$$

$$I_3 = 3 \text{ mA}$$

$$i_b = I_2 - I_1$$

$$= 5 - 5$$


$$= 0$$

Thus, $i_b = 0 \text{ mA}$.

chapter 4


LINEARITY AND SUPERPOSITION

- system is entity (hardware/software) that's characterized by input(s) (i.e. excitations/causes), output(s) (effects/responses), + description of relation(s) btwn inputs + outputs
 - ↳ SISO is single-input single-output system
- linear system has to satisfy 2 properties of homogeneity/scaling + additivity
- homogeneity property requires that if input is multiplied by constant, output must be multiplied by same constant
 - ↳ if input $x_1 = cx$, then output must be $y_1 = cy$ (for some constant c)
- additivity requires if y_1 is output due to input x_1 & y_2 is output due to input x_2 , then output due to input $x = x_1 + x_2$ is $y = y_1 + y_2$
- in circuits, input is independent voltage / current source & output is voltage/current somewhere in circuit

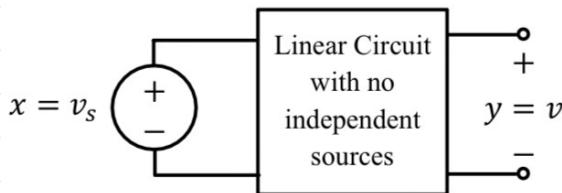

$$\hookrightarrow v = cv_s$$

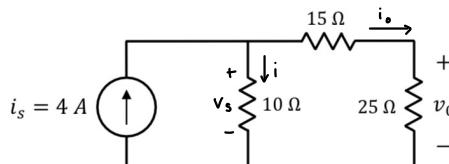- e.g. In the circuit shown below, find the actual voltage v_0 by assuming $v_0 = 1 V$ and using the linearity property.



SOLUTION

$$i_o = \frac{v_0}{25} = \frac{1}{25}$$

$$v_s = (15 + 25)i_o = \frac{40}{25}$$

$$i = \frac{v_s}{10} = \frac{4}{25}$$

$$i_s = i + i_o$$

$$= \frac{4}{25} + \frac{1}{25}$$

$$= \frac{1}{5} A$$

actual is assumed is

$$= \frac{4}{5}$$

$$= 20$$

$$V_0 = 20(1) = 20V$$


linearity doesn't apply to computation of power since it's non-linear function of current/voltage
 $\hookrightarrow P = VI = R I^2 = \frac{V^2}{R}$

- for linear circuits w/ 2+ independent current / voltage sources, linearity is applied through principle of superposition: current/voltage in linear circuit can be computed as algebraic sum of individual contributions of each independent source acting alone
- to deactivate independent sources:
 - ↳ voltage source $v_s = 0$: short circuit
 - ↳ current source $i_s = 0$: open circuit


- ↳ dependent sources aren't deactivated b/c they're not inputs to circuit system
- for DC circuits, superposition isn't always easier but for AC circuits w/ independent sources that have diff frequencies, superposition must be used

SOURCE TRANSFORMATION

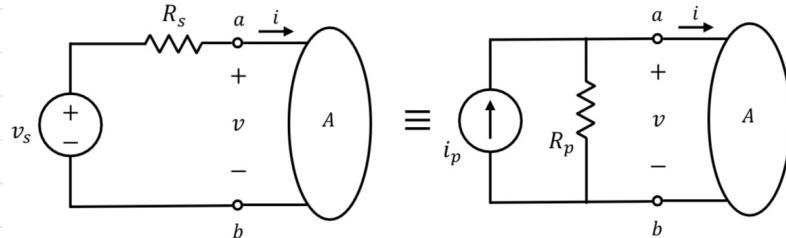- combo of voltage source in series w/resistance is equivalent to combo of current source in parallel w/resistance




- ↳ given i_p & R_p , can find v_s & R_s easily:
 - $R_s = R_p$
 - $v_s = R_p i_p$
- ↳ tip of arrow must point to terminal at which voltage source has the polarity
- ↳ source transformation can be applied to independent sources but control variable must be kept visible in circuit
- resistor in parallel w/voltage source & resistor in series w/current source have no effect on rest of circuit
- e.g. Find the voltage v_o using source transformation.

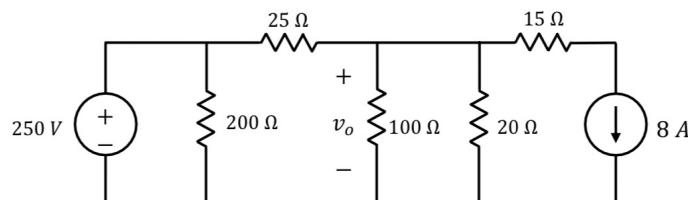


SOLUTION

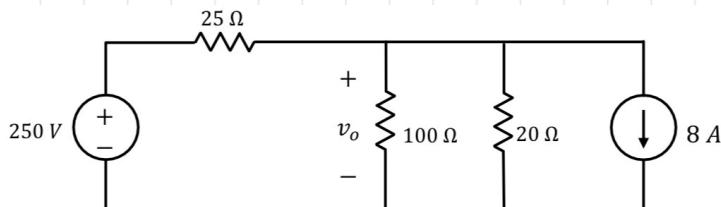- ↳ no source transformation on 250V in parallel w/ 200Ω + on 8A in series w/ 15Ω
- ↳ replace 200Ω w/open circuit + 15Ω w/short circuit



- ↳ use source transformation:

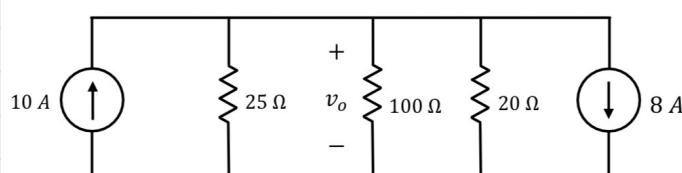

$$\circ 10A = \frac{250V}{25\Omega}$$

- ↳ combine 2 current sources + all resistors

$$\circ I_T = 10 - 8 \\ = 2A$$

$$\bullet \frac{1}{R_{eq}} = \frac{1}{25} + \frac{1}{100} + \frac{1}{20}$$

$$R_{eq} = 10 \Omega$$


$$\bullet V_o = I_T R_{eq}$$

$$= 2(10)$$


$$= 20 V$$

THEVENIN AND NORTON EQUIVALENT CIRCUITS

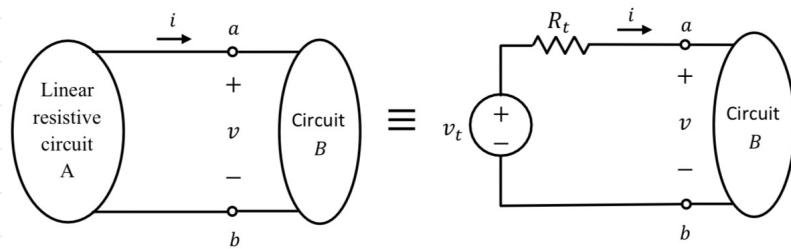- Thevenin's Theorem: any resistive linear circuit b/wn 2 terminals is equivalent to an independent voltage source in series w/ resistance




- from open-circuit:

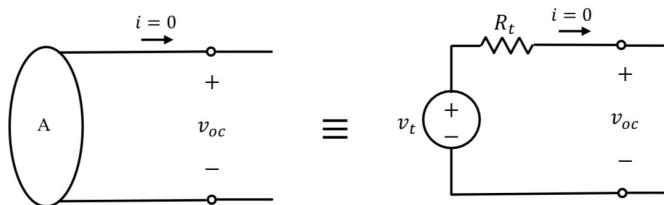

↳ since $i=0$, then $v_t = v_{oc}$

- from short-circuit:

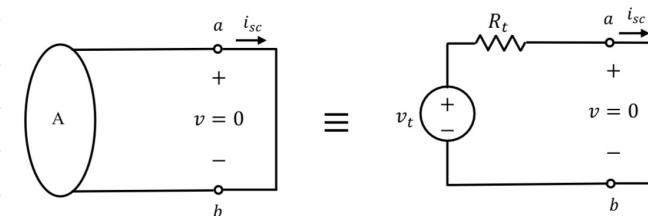


↳ since $v = 0$, $i_{sc} = \frac{v_t}{R_t} = \frac{V_{oc}}{R_t}$

$$\bullet R_t = \frac{V_{oc}}{i_{sc}}$$

- to ensure relations are tve, polarity of v_t should correspond to polarity of v_{oc} & dir of i_{sc} must be from tve to -ve of v_{oc} through short

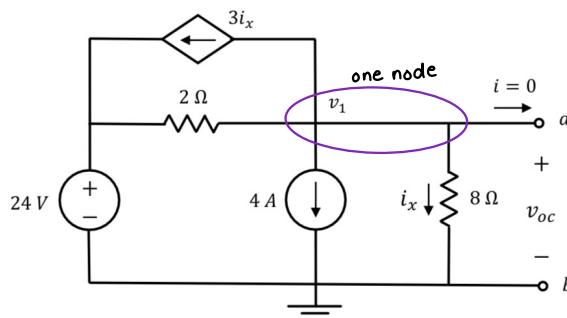- e.g. Find Thevenin equivalent circuit between the terminals a and b.



SOLUTION


Find v_{oc} w/open-circuit.

$$V_{oc} = V_1, i_x = \frac{V_1}{8}$$

$$\begin{aligned} \text{KCL at } v_1 : 0 &= 3i_x + \frac{v_1 - 24}{2} + 4 + i_x \\ 0 &= \frac{3v_1}{8} + \frac{v_1}{2} - 12 + 4 + \frac{v_1}{8} \\ 0 &= v_1 - 8 \\ v_1 &= 8V \end{aligned}$$

$$v_t = v_1 = V_{oc} = 8V$$

Find i_{sc} w/short-circuit.

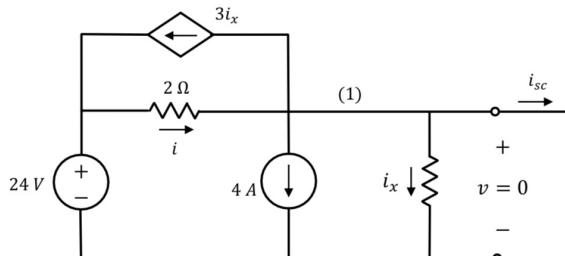

Since $v=0$, then $i_x = 0 \Rightarrow 3i_x = 0$ b/c i_x is in parallel w/short-circuit.


$$\text{KCL at node 1: } 0 = -i + 3i_x + 4 + i_{sc}$$

$$0 = -i + 4 + i_{sc}$$


$$\begin{aligned} i_{sc} &= i - 4 \\ &= \frac{24}{2} - 4 \\ &= 8A \end{aligned}$$

$$\begin{aligned} R_t &= \frac{V_{oc}}{i_{sc}} \\ &= \frac{8}{8} \\ &= 1\Omega \end{aligned}$$

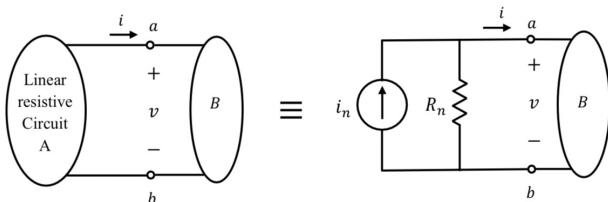Norton's Theorem: any resistive linear circuit btwn 2 terminals is equivalent to current source in parallel w/resistance



from short-circuit.

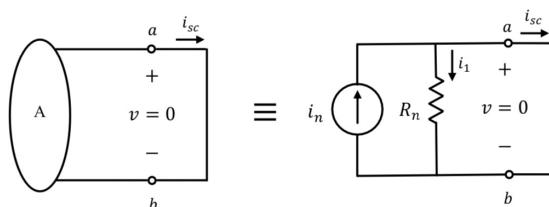


↳ since $v=0$:

$$\therefore i_1 = \frac{v}{R_n} = \frac{0}{R_n} = 0$$

$$\therefore i_{sc} = i_n - i_1$$

$$i_n = i_{sc}$$

from open-circuit:

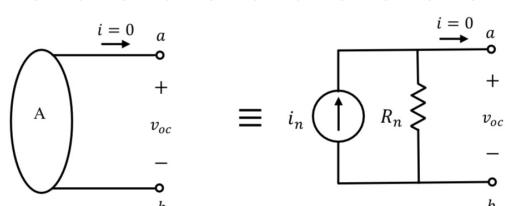


↳ since $i = 0$:

$$\circ V_{oc} = R_n \text{ in}$$

$$R_n = \frac{V_{oc}}{i_{sc}}$$

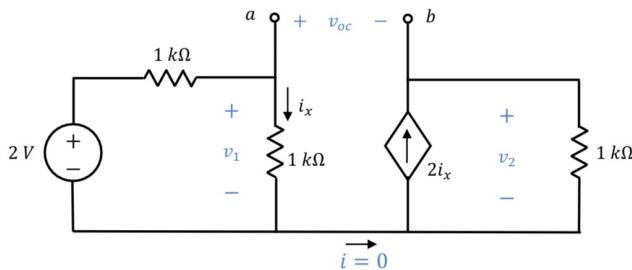- Thevenin & Norton equivalents are source transformation of each other
- when circuit has no independent sources, all currents & voltages are 0 so relation $R_T = R_n = \frac{V_{oc}}{i_{sc}}$ can't be applied
- e.g. Find Norton equivalent circuit between the terminals a and b .



SOLUTION

From open-circuit:

$$V_{oc} = V_1 - V_2$$

$$V_1 = 2 \left(\frac{1}{1+1} \right) \quad \leftarrow \text{voltage division}$$

$$= 1$$

$$V_2 = (2i_x)(1000)$$


$$= 2 \left(\frac{2}{1000+1000} \right) (1000)$$

$$= 2$$

$$V_{oc} = 1 - 2$$

$$= -1V$$

From short-circuit:

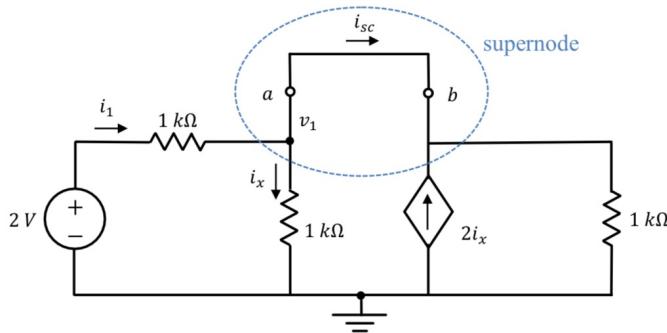

$$i_x = \frac{V_1}{1000}$$

$$\text{KCL at supernode: } 0 = \frac{V_1 - 2}{1000} + i_x - 2i_x + \frac{V_1}{1000}$$

$$0 = \frac{V_1}{1000} - \frac{2}{1000} - \frac{V_1}{1000} + \frac{V_1}{1000}$$

$$0 = -\frac{2}{1000} + \frac{V_1}{1000}$$

$$V_1 = 2V$$

$$0 = -i_1 + i_x + i_{sc}$$

$$i_{sc} = i_1 - i_x$$

$$= \frac{2-2}{1000} - \frac{2}{1000}$$


$$\approx -2mA$$

$$R_n = \frac{V_{oc}}{i_{sc}}$$


$$= \frac{-1V}{-2mA}$$

$$= 0.5k\Omega$$

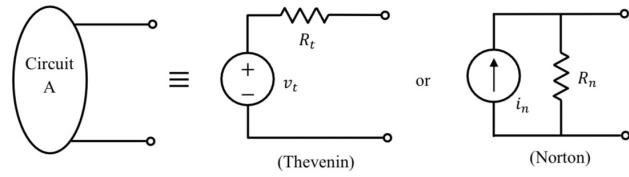- can find Thevenin/Norton resistance w/ equivalent resistance iff circuits have only independent sources



By deactivating the sources:

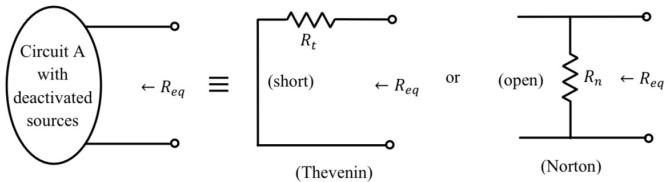

↳ for Thevenin:

- find v_{oc} as usual so $v_t = v_{oc}$
- R_{eq} from circuit A so $R_t = R_{eq}$

↳ for Norton:


- find i_{sc} as usual so $i_n = i_{sc}$
- R_{eq} from circuit A so $R_n = R_{eq}$

finding R_t or R_n using test source can be applied to any circuit w/independent i dependent sources


↳ deactivate all independent sources

↳ apply external test voltage source v_s or current source i_s

↳

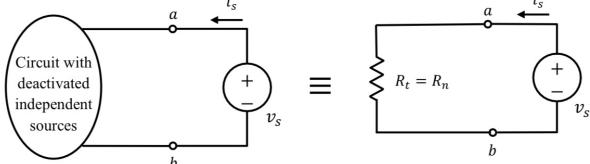

or

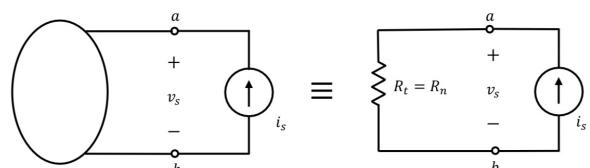


NOTE

- test source method must be used for circuits w/dependent sources only
- in this case, $v_{oc} = 0$ & $i_{sc} = 0$

↳ assume v_s/i_s & find the other value wrt assumed value, then $R_t = R_n = \frac{v_s}{i_s}$

MAXIMUM POWER TRANSFER (LOAD MATCHING)

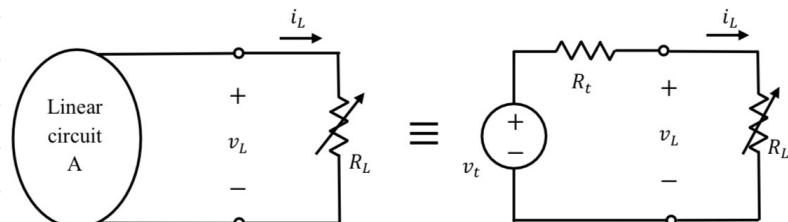- in many practical applications, given linear circuit is required to transfer max power to load resistance R_L
- replace linear circuit w/ Thevenin equivalent



power delivered by circuit A / absorbed by load R_L is $P_L = i_L^2 R_L$

$$= \left(\frac{V_t}{R_t + R_L} \right)^2 R_L$$

$$= \frac{V_t^2 R_L}{(R_t + R_L)^2}$$

to find R_L st P_L is max, differentiate wrt R_L & equate to 0.

$$\frac{dP_L}{dR_L} = \frac{V_t^2 (R_t + R_L)^2 - 2(R_t + R_L) V_t^2 R_L}{(R_t + R_L)^4} = 0$$

$$0 = V_t^2 (R_t + R_L)^2 - 2(R_t + R_L) V_t^2 R_L$$

$$0 = V_t^2 (R_t + R_L) (R_t + R_L - 2R_L)$$

$$0 = R_t - R_L$$

$R_{L\max} = R_t$

max power is $P_{L\max} = \frac{V_t^2 R_L}{(R_t + R_L)^2}$

$$= \frac{V_t^2 R_t}{(2R_t)^2}$$

$$P_{L\max} = \frac{V_t^2}{4R_t}$$

using Norton equivalent, $R_{L\max} = R_n$ & $P_{L\max} = \frac{R_n i_n^2}{4}$


chapter 5

OPERATIONAL AMPLIFIER


operational amplifier's main operations include amplification, addition, subtraction, differentiation, integration, & filtering

↳ aka op-amp

↳ symbol:

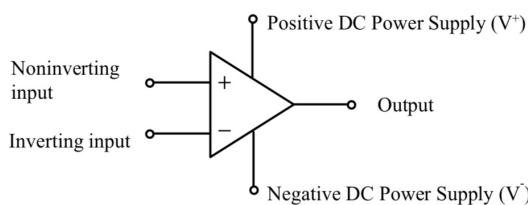

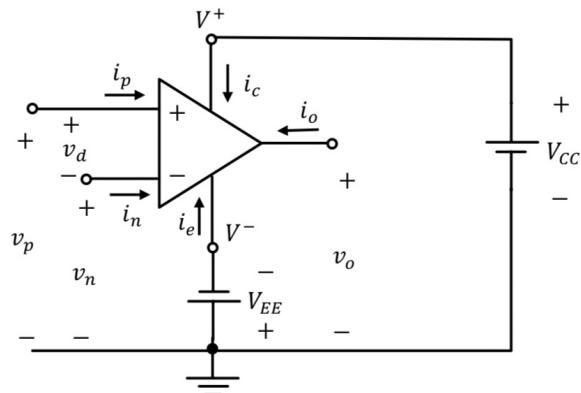terminal voltages & currents conventions:



↳ v_p & i_p rep noninverting input (+ve)

↳ v_n & i_n rep inverting input (-ve)

↳ v_o & i_o rep output

↳ V_{CC} & V_{EE} are batteries

↳ v_d is differential input voltage: $v_d = v_p - v_n$

◦ not a node voltage


· v_o is function of v_d :

$$v_o = \begin{cases} -V_{EE} & \text{for } Av_d < -V_{EE} \\ Av_d & \text{for } -V_{EE} \leq Av_d \leq +V_{CC} \\ +V_{CC} & \text{for } Av_d > +V_{CC} \end{cases} \quad \begin{array}{l} \text{(non-linear)} \\ \text{(linear)} \\ \text{(non-linear)} \end{array}$$

↳ A is open-circuit voltage gain (large constant)

◦ typical values of A : 10^5 to 10^8

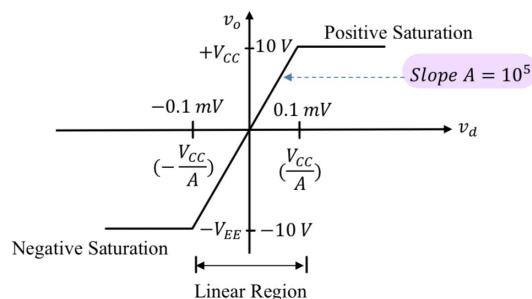↳ e.g. plot of v_o vs v_d w/ $V_{CC} = 10V$:




◦ linear region is actually very small

$$\text{for } A = 10^5 \text{ & } V_{CC} = 10V : \frac{V_{CC}}{A} = \frac{10V}{10^5} = 10^{-4}V = 0.1mV$$

- conclude that to operate op-amp in linear region, $|V_{OL}| \leq 0.1 \text{ mV}$
- condition for linear region in op-amp: $v_p \approx v_n$

NON-IDEAL LINEAR MODEL OF OP-AMP

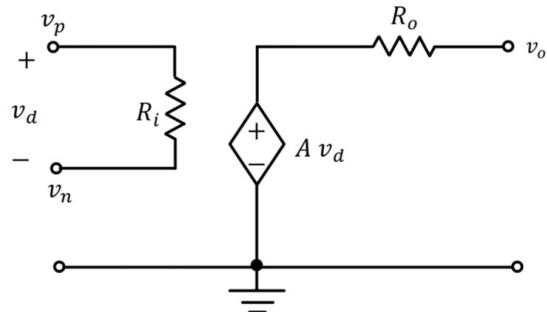- when $V_d = v_p - v_n$ is very small (i.e. $v_p \approx v_n$), op-amp can be modeled by linear circuit:




- ↳ 2 Thevenin equivalent circuits
- ↳ R_i is input resistance (very large)
 - typical values: 10^5 to $10^{12} \Omega$
- ↳ R_o is output resistance (very small)
 - typical values: 50 to 150 Ω
- ↳ A is open-circuit voltage gain (very large)
 - typical values: 10^5 to 10^8
- R_i , R_o , & A change widely w/ diff temps & aging
- feedback voltage from v_o to v_n (i.e. -ve feedback) is used b/c:
 - makes op-amp circuit invariant to parameter variations in R_i , R_o , & A
 - restricts operation in linear region
 - makes circuit more stable
- above linear model can be used to analyze any op-amp circuit, given that it's operating in linear region

e.g. Using the linear model:

(a) Find the voltage gain $G_v = \frac{v_o}{v_s}$

← inverting amplifier

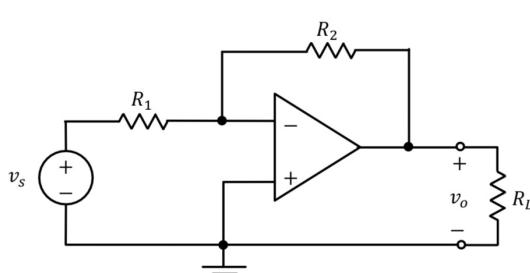(b) Compute v_o for $v_s = 1 \text{ V}$ and 0.5 V



$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 5 \text{ k}\Omega$$

$$R_L = 1 \text{ k}\Omega$$


$$R_i = 10^8 \Omega$$

$$R_o = 50 \Omega$$

$$A = 10^5$$

SOLUTION

Replace op-amp w/ its linear model:

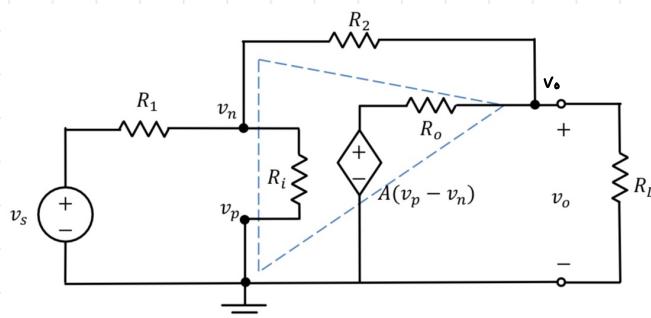

$$V_p = 0$$

$$\text{KCL at } V_n: 0 = \frac{V_n - V_s}{R_1} + \frac{V_n - V_p}{R_i} + \frac{V_n - V_o}{R_2}$$

$$\text{KCL at } V_o: 0 = \frac{V_o - V_n}{R_o} + \frac{V_o - V_n}{R_2} + \frac{V_o}{R_L}$$

Rearranging gives:

$$G_v = \frac{V_o}{V_s}$$

$$= -\frac{R_2}{R_1}$$

$$= \frac{\left(\frac{1}{R_1} + \frac{1}{R_i} + \frac{1}{R_2}\right)\left(\frac{1}{R_2} + \frac{1}{R_o}\right)}{\left(\frac{1}{R_2} + \frac{1}{R_o}\right) - \frac{1}{R_2}}$$

$$\approx -4.99968$$

$$\approx -5$$

NOTE

since A is very large (ideally, $A \rightarrow \infty$), then

$$\lim_{A \rightarrow \infty} \left(\frac{V_o}{V_s} \right) = -\frac{R_2}{R_1}$$

$$= -\frac{5k\Omega}{1k\Omega}$$

$$= -5$$

expression is independent of R_i , R_o , & A & can be derived more easily w/ ideal op-amp

For $V_s = 1V$:

$$V_o = G_v \times V_s$$

$$= 4.99968 (1V)$$

$$= -4.99968V$$

$$\approx -5V$$

For $V_s = -0.5V$:

$$V_o = G_v \times V_s$$


$$= 4.99968 (-0.5V)$$

$$= 2.49984V$$

$$\approx 2.5V$$

IDEAL OP-AMP MODEL

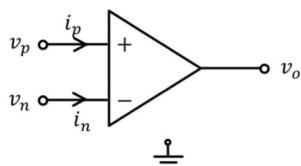- simple model that makes analysis of op-amp circuits easier



- derivation of model:

- R_i is very large (ideally, $R_i \rightarrow \infty$)

- $i_p = i_n = 0$

- input looks like open circuit


- voltage gain A is very large (ideally, $A \rightarrow \infty$)

- since $V_o = A(V_p - V_n)$ must be finite, then $V_p - V_n = 0$ (i.e. $V_p = V_n$)

- input looks like short circuit

↳ conditions rep assumptions for ideal op-amp

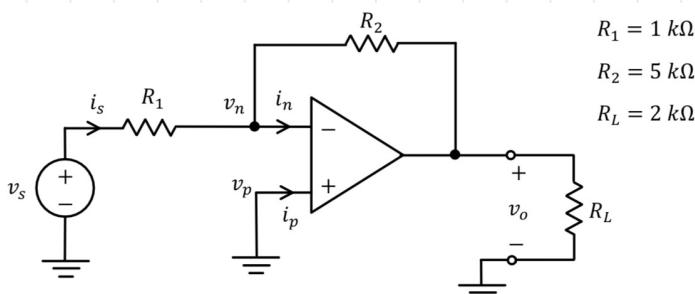e.g. same inverting amplifier but assume ideal op-amp



VOLTAGE GAIN ($G_v = \frac{V_o}{V_s}$)

↳ by circuit connection, $V_p = 0$

↳ by ideal op-amp, $V_n = V_p = 0$

↳ KCL at V_n : $0 = \frac{V_n - V_s}{R_1} + \frac{V_n - V_o}{R_2} + i_{in}$

$$0 = -\frac{V_s}{R_1} - \frac{V_o}{R_2}$$

$$V_o = -\frac{R_2}{R_1} V_s$$

← since $V_n = 0$ & $i_{in} = 0$

↳ $G_v = \frac{V_o}{V_s}$

$$= -\frac{R_2}{R_1} V_s \left(\frac{1}{V_s} \right)$$

$$G_v = -\frac{R_2}{R_1}$$

$$= -5$$

INPUT RESISTANCE (IMPEDANCE) ($R_{in} = \frac{v_s}{i_s}$)

↳ Thevenin equivalent resistance as seen by source

↳ KVL at input: $-v_s + R_1 i_s + v_n = 0$

$$v_s = R_1 i_s \quad \leftarrow \text{since } v_n = 0$$

$$R_1 = \frac{v_s}{i_s}$$

$$R_{in} = R_1$$

$$= 1 k\Omega$$

OUTPUT RESISTANCE

↳ Thevenin equivalent resistance as seen by load

↳ since $v_o = -\frac{R_2}{R_1} v_s$, regardless of R_L , then $R_{out} = 0$

• i.e. R_L sees perfect controlled voltage source

• even if R_L changes, v_o doesn't

↳ ideally, R_L has no effect on G_v , R_{in} , & R_{out}

• i.e. R_L is isolated from v_s

e.g. non-inverting amplifier


Assuming ideal op-amp, find:

(a) The voltage gain $G_v = \frac{v_o}{v_s}$.

(b) The voltage v_o and the current i_o for $v_s = 0.5 V$.

(c) The power supplied by the source v_s and the power absorbed by the load R_L for $v_s = 0.5 V$.

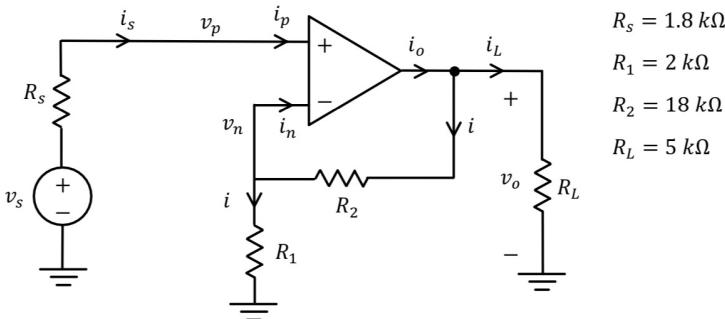(d) The input resistance $R_{in} = \frac{v_s}{i_s}$ seen by the source v_s and the output resistance R_{out} seen by the load R_L .



SOLUTION

a) By ideal op-amp: $v_n = v_p \quad \& \quad i_n = i_p = 0$

$$v_n = v_p = v_s - R_s i_p$$

$$= v_s - R_s (0)$$

$$= v_s$$

$$\text{KCL at } v_n: 0 = \frac{v_n}{R_1} + \frac{v_n - v_o}{R_2}$$

$$0 = v_n \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{v_o}{R_2}$$

$$\frac{v_o}{R_2} = v_n \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$v_o = R_2 v_n \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{v_o}{v_s} = R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$G_v = \frac{R_2}{R_1} + 1 \quad \leftarrow \text{independent of } R_L$$

$$= \frac{18}{2} + 1$$

$$= 10 \quad \leftarrow 10 \times \text{amplification}$$

b) $v_o = G_v v_s = 10 (0.5 V)$

$$= 5 V$$

$$0 = -i_o + i + i_L$$

$$\begin{aligned} i_o &= i + i_L \\ &= \frac{V_o}{R_1 + R_2} + \frac{V_o}{R_L} \\ &= \frac{5}{2+18} + \frac{5}{5} \\ &= 1.25 \text{ mA} \end{aligned}$$

← since i_n is open circuit, other ways to rep i are $\frac{V_o - V_n}{R_2}$ or $\frac{V_n}{R_1}$

c) $P_s = V_s i_s = V_s i_p = 0 \text{ W}$

$$\begin{aligned} P_L &= \frac{V_o^2}{R_L} \\ &= \frac{5^2}{5k} \end{aligned}$$

= 5 mW ← very large power gain (comes from DC)

d) Since $i_s = i_p = 0$, then:


$$\hookrightarrow R_{in} = \frac{V_s}{i_s} = \frac{V_s}{0} \rightarrow \infty$$

• very large

$$\hookrightarrow R_{out} = R_t = 0$$

• b/c V_o is independent of R_L

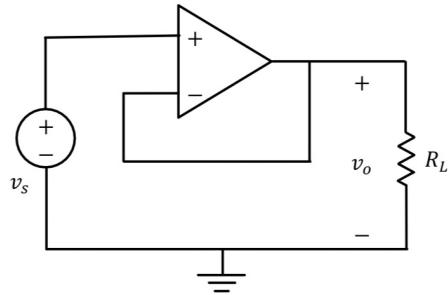· for $R_1 = \infty$ & $R_2 = 0$ of above non-inverting amplifier, we get unity-gain buffer




NOTE

· for summing amplifier,
 $v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2\right)$
 can be applied to any # of input sources

↳ used when source needs to be isolated from effect of change of load

· e.g. cascading op-amp circuit

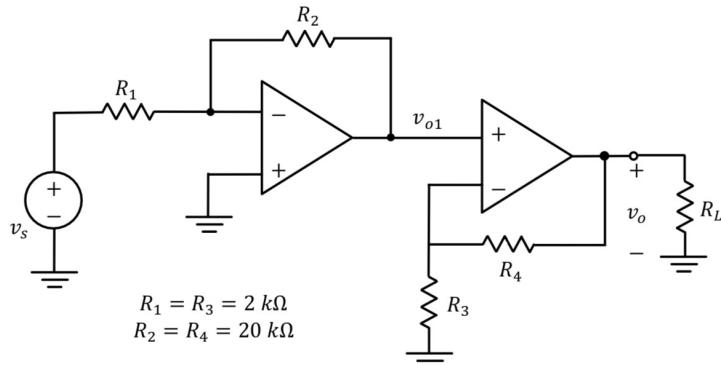Find the voltage gain = $\frac{v_o}{v_s}$, assuming ideal op-amp.



SOLUTION

↳ circuit is cascade of inverting amplifier & non-inverting amplifier

First op-amp: $V_{o1} = -\frac{R_2}{R_1} V_s$

Second op-amp: $V_o = (1 + \frac{R_4}{R_3}) V_{o1}$

$$V_o = (1 + \frac{R_4}{R_3})(-\frac{R_2}{R_1}) V_s$$

$$\frac{V_o}{V_s} = -\frac{R_2}{R_1} (1 + \frac{R_4}{R_3})$$

$$G = -\frac{R_2}{R_1} (1 + \frac{R_4}{R_3})$$

$$= -10(1+10)$$


$$= -110$$

↳ voltage gain is product of 2 op-amps' voltage gains

chapter 6

CAPACITOR

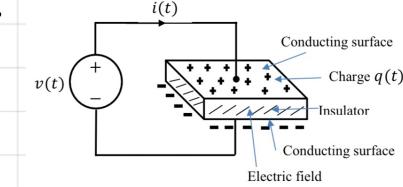
- capacitor consists of 2 conducting surfaces separated by insulator



- ↳ e⁻ move from voltage source to be collected on lower plate as charge q(t)
 - creates E-field which forces e⁻ to leave upper plate & make it +ve w/ charge q(t)

- ↳ capacitor energy stored in its E-field can be later supplied to outside circuit

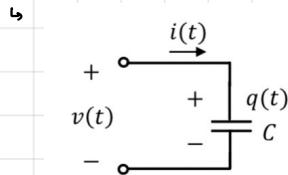ideal linear capacitor has following linear relation for charge: $q(t) = C v(t)$



- ↳ q(t) = charge in Coulombs (C)

- ↳ v(t) = voltage in Volts (V)

- ↳ C = capacitance in Farad ($1 \text{ F} = \frac{1 \text{ C}}{1 \text{ V}}$)

- constant that depends on physical dimensions of capacitor & material of insulator

- practical capacitors have range of $1 \text{ pF} (10^{-12} \text{ F})$ to $10000 \mu\text{F} (10^{-6} \text{ F})$

taking derivative of above relation gives $i(t) = \frac{dq(t)}{dt} = C \frac{dv(t)}{dt}$

- ↳ if capacitor doesn't comply w/ PSC (i.e. current goes from +ve to -ve), $i(t) = -C \frac{dv(t)}{dt}$

- ↳ if voltage v(t) is constant (i.e. DC voltage), then $i(t) = 0$

- i.e. capacitor looks like open circuit

- ↳ capacitor voltage must be continuous function of time

- can't have jump since $\frac{dv(t)}{dt}$ isn't defined there & infinite current is required

- ↳ capacitor current can have jump

- to find v(t) from i(t):

$$\hookrightarrow \text{from } i(t) = C \frac{dv(t)}{dt}, dv(t) = \frac{1}{C} i(t) dt$$

$$\hookrightarrow \text{change of variables } (t \rightarrow \tau) : dv(\tau) = \frac{1}{C} i(\tau) d\tau$$

$$\hookrightarrow \text{integrate from } \tau = t_0 \text{ to } \tau = t : \int_{v(t_0)}^{v(t)} dv(\tau) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$v(t) - v(t_0) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

- power can be defined as $p(t) = v(t) i(t) = C v(t) \frac{dv(t)}{dt}$

- to find energy:

$$\hookrightarrow p(t) = \frac{dw(t)}{dt}$$

$$dw(t) = p(t) dt$$

$$\hookrightarrow \text{change of variables } (t \rightarrow \tau) : dw(\tau) = p(\tau) d\tau$$

$$\hookrightarrow \text{energy delivered to capacitor from } \tau = t_1 \text{ to } \tau = t_2 :$$

$$\int_{w(t_1)}^{w(t_2)} dw(\tau) = \int_{t_1}^{t_2} p(\tau) d\tau$$

$$\int_{w(t_1)}^{w(t_2)} dw(\tau) = \int_{t_1}^{t_2} C v(\tau) \frac{dv(\tau)}{d\tau} d\tau$$

$$w(t_2) - w(t_1) = C \int_{v(t_1)}^{v(t_2)} v(\tau) dv(\tau)$$

$$w(t_2) - w(t_1) = C \left[\frac{1}{2} v^2(t_2) - \frac{1}{2} v^2(t_1) \right]$$

$$w = \frac{1}{2} C (v^2(t_2) - v^2(t_1))$$

- rep. energy stored in capacitor from t_1 to t_2 $\frac{q^2(t)}{2C}$
- energy as function of time is $w(t) = \frac{1}{2} Cv^2(t) = \frac{q^2(t)}{2C}$

INDUCTOR


inductor consists of conducting wire in form of coil

↳ usually coil wound around iron core

↳ stores energy in magnetic field

- voltage of ideal linear conductor is $v(t) = L \frac{di(t)}{dt}$

↳

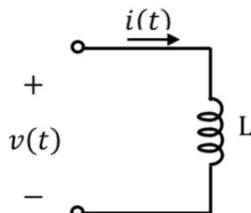

↳ $L = \text{inductance in Henry (H)} = \frac{Vs}{A}$

• constant that depends on physical dimensions of inductor, # of coil turns, & material of core

• practical inductors have range of a few μH to tens of H

- if $i(t)$ is constant (i.e. DC current), then $v(t) = 0$

• i.e. inductor looks like short circuit

↳ inductor current must be continuous function of time

↳ can't have jump since $\frac{di(t)}{dt}$ isn't defined there & infinite voltage is required

- inductor relations are similar to capacitor relations but w/ replacements of $v(t) \rightarrow i(t)$, $i(t) \rightarrow v(t)$, &

$$C \rightarrow L$$



$$\hookrightarrow i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

$$\hookrightarrow \text{power: } p(t) = v(t) i(t) = L i(t) \frac{di(t)}{dt}$$

$$\hookrightarrow \text{stored energy from } t_1 \text{ to } t_2: w = w(t_2) - w(t_1) = \frac{1}{2} L (i^2(t_2) - i^2(t_1))$$

$$\hookrightarrow \text{stored energy as function of } t: w(t) = \frac{1}{2} L i^2(t)$$

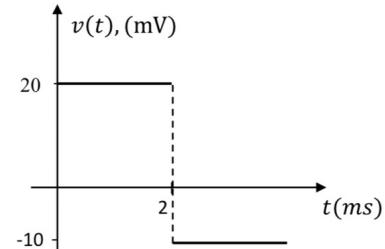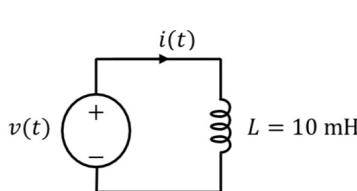e.g. Find $i(t)$ and $w(t)$ for $t \geq 0$, assuming $i(0^-) = 0$.



SOLUTION

For $0 \leq t < 2 \text{ ms}$:

$$\hookrightarrow t_0 = 0$$

↳ $i(0) = i(0^-) = 0$ b/c current is continuous function

$$\begin{aligned} i(t) &= \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0) \\ &= \frac{1}{10 \cdot 10^{-3}} \int_0^t 20 \cdot 10^{-3} d\tau + 0 \end{aligned}$$

$$i(t) = 2t \text{ A}$$

$$\text{At } t = 2^- \text{ ms}, i(2^- \text{ ms}) = 2(2 \cdot 10^{-3})$$

$$= 4 \cdot 10^{-3} \text{ A}$$

For $2 \text{ ms} \leq t < \infty$:

$$\hookrightarrow t_0 = 2 \text{ ms}$$


$$\hookrightarrow i(2 \text{ ms}) = i(2^- \text{ ms}) = 4 \cdot 10^{-3} \text{ A}$$

$$i(t) = \frac{1}{10 \cdot 10^{-3}} \int_{2 \cdot 10^{-3}}^t (-10 \cdot 10^{-3}) d\tau + i(2 \text{ ms})$$


$$= -(t - 2 \cdot 10^{-3}) + 4 \cdot 10^{-3}$$

$$i(t) = -t + 6 \cdot 10^{-3} \text{ A}$$

$i(t), (\text{mA})$

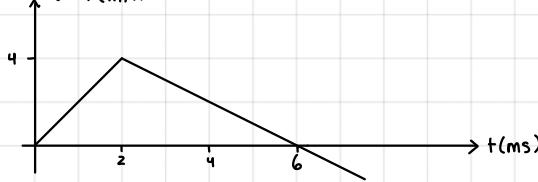

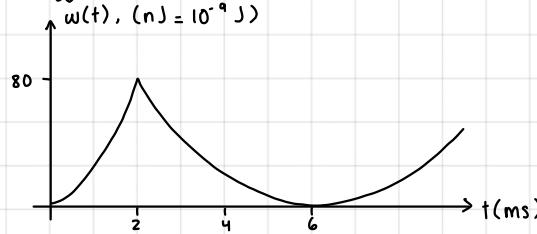
$$\text{Energy: } w(t) = \frac{1}{2} L i^2(t)$$



$$w(t) = \begin{cases} (20 \cdot 10^{-9}) t^2, & 0 \leq t \leq 2 \text{ ms} \\ \frac{1}{2} (10 \cdot 10^{-3})(-t + 6 \cdot 10^{-3})^2, & 2 \text{ ms} \leq t \end{cases}$$


e.g.

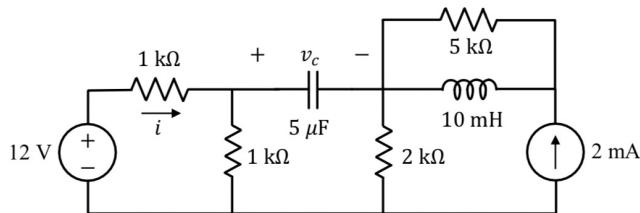

- Find the current i and the voltage v_c .
- Find the energy stored in each of L and C .

SOLUTION

DC equivalent circuit:

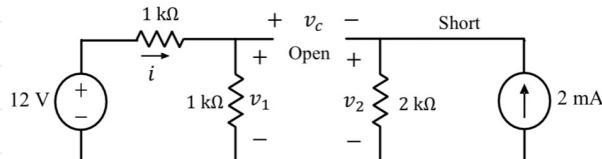

$\hookrightarrow L$ is short $\&$ C is open

$$i = \frac{12 \text{ V}}{1\text{k}+1\text{k}} = 6 \text{ mA} \quad v_1 = 1\text{k} (6 \text{ mA}) = 6 \text{ V} \quad v_2 = 2\text{k} (2 \text{ mA}) = 4 \text{ V} \quad v_c = v_1 - v_2 = 6 - 4 = 2 \text{ V}$$

$$W_L = \frac{1}{2} L i_L^2$$

$$= \frac{1}{2} (10 \text{ mH}) (2 \text{ mA})^2$$

$$= 20 \cdot 10^{-9} \text{ J}$$

$$= 20 \text{ nJ}$$

$$W_C = \frac{1}{2} C v_c^2$$


$$= \frac{1}{2} (5 \mu\text{F}) (2)^2$$

$$= 10 \cdot 10^{-6} \text{ J}$$

$$= 10 \mu\text{J}$$

PARALLEL AND SERIES CAPACITORS

parallel capacitors:

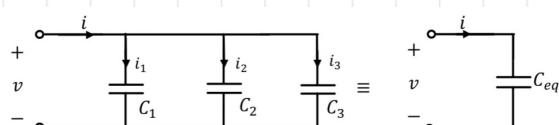

\hookrightarrow use KCL: $i = i_1 + i_2 + i_3$


$$= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt}$$

$$= (C_1 + C_2 + C_3) \frac{dv}{dt}$$

↳ $C_{eq} = C_1 + C_2 + C_3$

◦ i.e. capacitors in parallel are added


· series capacitors:

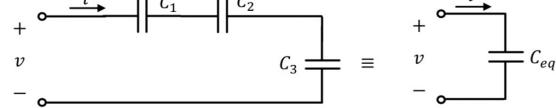

↳ $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$

◦ similar to resistors in parallel

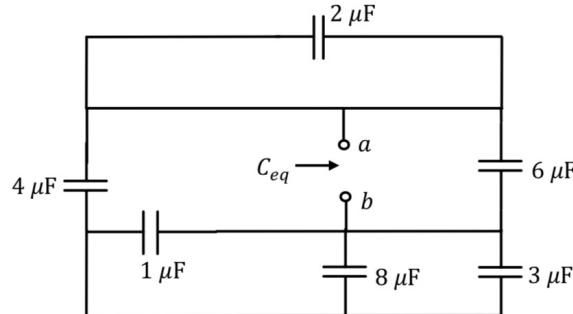· e.g. Find equivalent capacitance C_{eq} between a and b .



SOLUTION

↳ 2 μF is in parallel w/ short

↳ 1 μF, 8 μF, & 3 μF are in parallel w/ one another

$$C_x = 1 \mu F \parallel 8 \mu F \parallel 3 \mu F$$

$$= 1 + 8 + 3$$

$$= 12 \mu F$$


↳ 4 μF is in series w/ C_x , which in turn is in parallel w/ 6 μF

$$C_{eq} = \frac{4 \cdot 12}{4+12} + 6$$

$$C_{eq} = 9 \mu F$$

SERIES AND PARALLEL INDUCTORS

· series inductors:

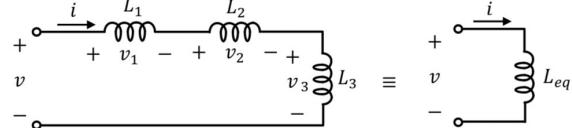


↳ use KVL: $v = v_1 + v_2 + v_3$

$$\begin{aligned} &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} \\ &= (L_1 + L_2 + L_3) \frac{di}{dt} \end{aligned}$$

↳ $L_{eq} = (L_1 + L_2 + L_3)$

◦ inductors in series are added

· parallel inductors:

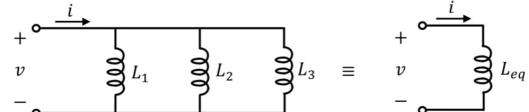


↳ $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$

◦ similar to resistors in parallel

chapter 7

DISCHARGING OF RC CIRCUIT

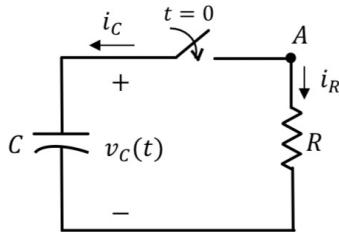- time-varying currents & voltages resulting from abrupt change of circuit / due to switching are called transients
- generally, transient analysis requires solving differential equations



- before $t=0$, capacitor is assumed to be charged to initial voltage V_i
 - i.e. $v_C(0^-) = V_i$
- at $t=0$, switch closes & $v_C(0) = v_C(0^-) = V_i$
- for $t \geq 0$, current flows thru resistor discharging capacitor
 - eventually, all energy will be dissipated from resistor

SOLUTION

KCL at node A:

$$i_C + i_R = 0$$

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} = 0, \quad t \geq 0$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 0 \quad \leftarrow 1^{\text{st}} \text{ order differential equation (DE)}$$

solution of DE $v_C(t)$ must be function that has form that's similar to its derivative so exponential function ($y = e^{st}$) satisfies requirement

assume $v_C(t) = Ke^{st}$, $t \geq 0$

$\circ K$ & s are constants

$$\frac{dv_C(t)}{dt} = Kse^{st}$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 0$$

$$RCKse^{st} + Ke^{st} = 0$$

$$Ke^{st}(RCst + 1) = 0$$

for non-trivial solution $Ke^{st} \neq 0$, then $RCst + 1 = 0$

$$s = -\frac{1}{RC}$$

$$v_C(t) = Ke^{st}$$

$$v_C(t) = Ke^{-\frac{t}{RC}}$$

find K from initial condition: $v_C(0) = V_i$

$$V_i = Ke^{-\frac{0}{RC}}$$

$$K = V_i$$

Solution is $v_C(t) = V_i e^{-\frac{t}{RC}}$, $t \geq 0$

rapidity of decay is constant $\gamma = RC$

γ is time-constant of circuit

response decays faster for smaller γ

$$v_C(t) = V_i e^{-\frac{t}{\gamma}}, \quad t \geq 0$$

theoretically, capacitor will never be completely discharged but practically, we assume it is

when $v_c(t) \approx 0$

↳ e.g. for $t > 5\tau$, capacitor assumed to be completely discharged

· discharging of RC circuit aka source-free RC circuit

· current thru capacitor is: $i_c(t) = C \frac{dv_c(t)}{dt}$

$$= -C \frac{V_i}{\tau} e^{-\frac{t}{\tau}}$$

$$= -C \frac{V_i}{RC} e^{-\frac{t}{\tau}}$$


$$i_c(t) = -\frac{V_i}{R} e^{-\frac{t}{\tau}}, t \geq 0$$

↳ jump at $t=0$, where $i_c(0^-) = 0 \Rightarrow i_c(0) = -\frac{V_i}{R}$


· energy w_R that's dissipated by R from $t: 0 \rightarrow \infty$ is equal to initial energy w_C stored in capacitor

↳ i.e. $w_R = w_C = \frac{1}{2} CV_i^2$

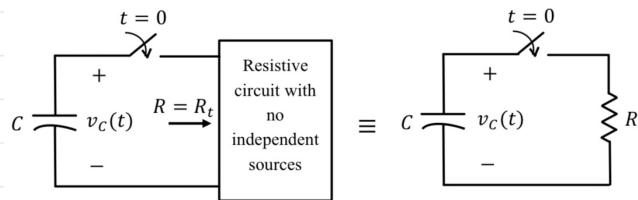R in RC circuit can be Thevenin equivalent resistance of any circuit w/no independent sources



CHARGING RC CIRCUIT

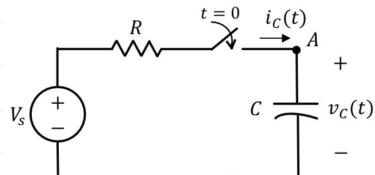

↳ source is DC source so $V_s = \text{constant}$

↳ capacitor is assumed to be initially discharged so $v_c(0^-) = 0$

↳ at $t=0$, switch closes $\Rightarrow v_c(0) = v_c(0^-) = 0$

↳ for $t \geq 0$, current flows charging capacitor

SOLUTION

KCL at node A:

$$\frac{v_c(t) - V_s}{R} + \frac{i_c(t)}{C} = 0$$

$$C \frac{dv_c(t)}{dt} + \frac{v_c(t) - V_s}{R} = 0$$

$$RC \frac{dv_c(t)}{dt} + v_c(t) = V_s, t \geq 0 \quad \leftarrow 1^{\text{st}} \text{ order DE}$$

↳ since RHS is constant, then assume solution: $v_c(t) = K_1 + K_2 e^{st}$

° K_1, K_2, s are constants

$$RC \frac{dv_c(t)}{dt} + v_c(t) = V_s$$

$$RC K_2 s e^{st} + K_1 + K_2 e^{st} = V_s$$

$$K_2 e^{st} (RCs + 1) + K_1 = V_s$$

↳ match functions on both sides:

° $K_1 = V_s$

° $(RCs + 1) K_2 e^{st} = 0$

$$RCs + 1 = 0$$

$$s = -\frac{1}{RC}$$

↳ find K_2 from initial condition: $v_c(0) = 0$

$$0 = K_1 + K_2 e^{st} \Big|_{t=0}$$

$$0 = V_s + K_2 e^{-\frac{0}{RC}}$$

$$K_2 = -V_s$$

Solution is $v_c(t) = V_s - V_s e^{-\frac{t}{RC}} = V_s(1 - e^{-\frac{t}{\tau}})$, $t \geq 0$

↳ $\tau = RC$ is time-constant

· for $t > 5\tau$, capacitor is assumed practically to be completely charged

↳ i.e. $v_c(t) \approx V_s$

↳ DC value V_s is called DC steady-state value of $v_c(t)$

charging of RC circuit aka step response of RC circuit

· current thru capacitor is given by: $i_c(t) = C \frac{dv_c(t)}{dt}$

$$= C \frac{V_s}{\tau} e^{-\frac{t}{\tau}}$$

$$= C \frac{V_s}{RC} e^{-\frac{t}{\tau}}$$

$$i_c(t) = \frac{V_s}{R} e^{-\frac{t}{\tau}}, t \geq 0$$

↳ jump at $t=0$, where $i_c(0^-) = 0 \Rightarrow i_c(0) = \frac{V_s}{R}$

· if initial value is non-zero (i.e. $v_c(0^-) = V_i$), then complete solution is $v_c(t) = V_s + (V_i - V_s)e^{-\frac{t}{\tau}}$, $t \geq 0$

· complete solution for any circuit can be decomposed into 2 components: $v_c(t) = v_{ss}(t) + v_{tr}(t)$

↳ $v_{ss}(t)$ is steady-state response, which persists forever

◦ e.g. V_s in above RC circuit

↳ $v_{tr}(t)$ is transient response, which decays to 0 after a long time

◦ e.g. $(V_i - V_s)e^{-\frac{t}{\tau}}$ in above RC circuit

· instead of specifying equation is valid for $t \geq 0$, step function $u(t)$ is used

↳ $u(t) = \begin{cases} 1, & t \geq 0 \\ 0, & t < 0 \end{cases}$

↳ rewrite function as $v_c(t) = [V_s + (V_i - V_s)e^{-\frac{t}{\tau}}] u(t)$

· if switch closes at time $t = t_0$ instead of $t = 0$, complete solution becomes $v_c(t) = V_s + (V_i - V_s)e^{-\frac{t-t_0}{\tau}}$, $t \geq t_0$

· instead of solving differential equation for every 1st order RC circuit, use general solution:

$$v_c(t) = v_c(\infty) + [v_c(t_0) - v_c(\infty)] e^{-\frac{t-t_0}{\tau}}, t \geq t_0$$

↳ $v_c(\infty)$ is final value / DC steady-state value when $t \rightarrow \infty$


↳ $v_c(t_0)$ is initial value

↳ $\tau = RC$ is time-constant

↳ can be applied for both charging & discharging RC circuits

· if capacitor's connected to more complicated linear circuit, use Thevenin equivalent

↳

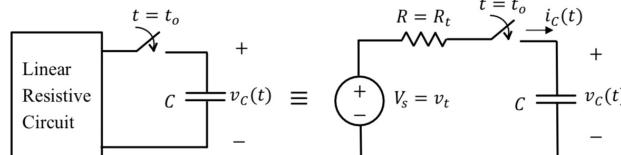


↳ in general solution:

◦ $v_c(\infty) = V_t$

◦ $\tau = R_t \cdot C$

RL CIRCUIT

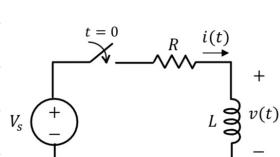

TIP

for RL circuit,
always find eq
for $i(t)$ first then
derive $v(t)$ from it

↳ assume $V_s = \text{constant}$ & $i(0^-) = 0$

↳ at $t = 0$, switch closes & $i(0) = i(0^-) = 0$ b/c no jump

↳ for $t \geq 0$, current flows thru $R \parallel L$

SOLUTION

Using KVL: $Ri(t) + L \frac{di(t)}{dt} = V_s$
 $\frac{L}{R} \frac{di(t)}{dt} + i(t) = \frac{V_s}{R}, t \geq 0$

↳ DE has same form as prev DE from RC circuit w/replacements:

- $v_c(t) \rightarrow i(t)$

- $RC \rightarrow \frac{L}{R}$

- $V_s \rightarrow \frac{V_s}{R}$

Solution is $i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-\frac{t}{\tau}}$, $t \geq 0$

↳ $\tau = \frac{L}{R}$ is time-constant of RL circuit

· to find voltage: $v(t) = L \frac{di(t)}{dt}$
 $= L \left(\frac{V_s}{R\tau} e^{-\frac{t}{\tau}} \right)$
 $v(t) = V_s e^{-\frac{t}{\tau}}, t \geq 0$

↳ at $t=0$, inductor behaves as open circuit since $v(0) = V_s$

↳ after long time, inductor behaves as short circuit (i.e. $v(t) = 0$)

· general solution for RL circuit: $i(t) = i(\infty) + [i(t_0) - i(\infty)] e^{-\frac{t-t_0}{\tau}}, t \geq t_0$


↳ $i(\infty)$ is final value / DC steady-state of inductor current

↳ $i(t_0)$ is initial current value

↳ $\tau = \frac{L}{R}$ is time-constant

- R is Thevenin Req as seen by inductor

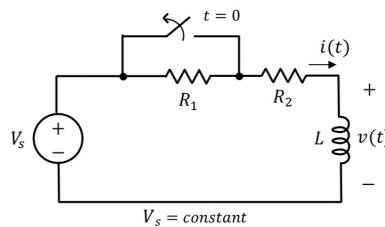· e.g. Assume switch is closed for a long time before $t = 0$. Find $i(t)$ and $v(t)$ for $t \geq 0$.




SOLUTION


For $t = 0^-$, switch is closed & circuit's in DC steady-state

↳ $i(0^-) = \frac{V_s}{R_2}$

↳ $v(0^-) = 0$

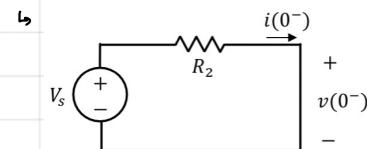

For $t \geq 0$, switch is open:

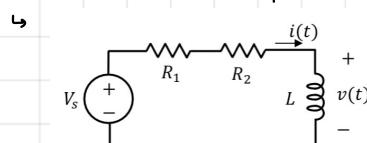

↳ $t_0 = 0$

↳ $i(0) = i(0^-) = \frac{V_s}{R_2}$ b/c no jump

↳ $i(\infty) = \frac{V_s}{R_1 + R_2}$

- inductor becomes short circuit again & circuit's at DC steady-state

↳ $\tau = \frac{L}{R}$
 $= \frac{L}{R_1 + R_2}$

Subbing values into general formula:

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-\frac{t}{\tau}}, t \geq 0$$

$$i(t) = \frac{V_s}{R_1+R_2} + \left[\frac{V_s}{R_2} - \frac{V_s}{R_1+R_2} \right] e^{-\frac{t}{\tau}}, t \geq 0$$

$$\hookrightarrow \tau = \frac{L}{R_1+R_2}$$

To find voltage:

$$v(t) = L \frac{di(t)}{dt}$$

$$= -\frac{L}{\tau} \left[\frac{V_s}{R_2} - \frac{V_s}{R_1+R_2} \right] e^{-\frac{t}{\tau}}$$

$$= -\frac{L}{R_1+R_2} \left[\frac{V_s}{R_2} - \frac{V_s}{R_1+R_2} \right] e^{-\frac{t}{\tau}}$$


$$= (R_1+R_2) \left(\frac{V_s}{R_1+R_2} - \frac{V_s}{R_2} \right) e^{-\frac{t}{\tau}}$$

$$v(t) = -V_s \frac{R_1}{R_2} e^{-\frac{t}{\tau}}, t \geq 0$$

chapter 8

SINUSOIDS

- sinusoidal current is usually called Alternating Current (AC)
 - ↳ electric circuits w/ sinusoidal current &/or voltage sources are called AC circuits
- for AC circuits, transient component ($v_{tr}(t)$) isn't important b/c it decays to 0 quickly
 - ↳ only consider steady-state analysis of AC circuits
- everlasting sinusoidal voltage is $v(t) = V_m \cos(\omega t + \theta)$, $-\infty < t < \infty$
 - ↳ V_m is amp, peak, or max value of sinusoid
 - ↳ ω is angular freq
 - radians/s
 - ↳ θ is phase angle
 - rads
- period of sinusoid is $T = \frac{2\pi}{\omega}$ s
- frequency is $f = \frac{1}{T}$ cycles/s (Hertz)
 - ↳ $\omega = \frac{2\pi}{T} = 2\pi f$
- useful math formulas:
 - ↳ $\sin \alpha = \cos(\alpha - \frac{\pi}{2})$
 - ↳ $-\sin \alpha = \cos(\alpha + \frac{\pi}{2})$
 - ↳ $-\cos \alpha = \cos(\alpha \pm \pi)$
 - ↳ $\sin(\alpha + \beta) = \sin \alpha \cos \beta + \cos \alpha \sin \beta$
 - ↳ $\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$
- complex # z defined in rectangular form is $z = x + jy$
 - ↳ $x = \text{Re}[z]$ is real part
 - ↳ $y = \text{Im}[z]$ is imaginary part
 - ↳ $j = \sqrt{-1}$ is imaginary operator
- complex # rep graphically:

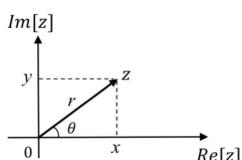

- complex # in polar form is $z = r \angle \theta$
 - ↳ $r = |z| = \sqrt{x^2 + y^2}$ is magnitude
 - ↳ $\theta = \angle z = \tan^{-1}(\frac{y}{x})$ is angle
- complex # in exponential form is $z = r e^{j\theta}$
 - ↳ using Euler's identity $e^{j\theta} = \cos \theta + j \sin \theta$, can convert exp form to rectangular form:
$$z = r e^{j\theta}$$
$$z = r \cos \theta + j r \sin \theta$$
 - $x = r \cos \theta$
 - $y = r \sin \theta$
- polar & exp form are essentially same b/c both are specified by r & θ
- since $j = \sqrt{-1}$:
 - ↳ $j^2 = -1$

$$\hookrightarrow j^3 = -j$$

$$\hookrightarrow j^4 = 1$$

$$\hookrightarrow \frac{1}{j} = -j$$

· using Euler's identity:

$$\hookrightarrow \cos\theta = \frac{1}{2}(e^{j\theta} + e^{-j\theta})$$

$$\hookrightarrow \sin\theta = \frac{1}{2j}(e^{j\theta} - e^{-j\theta})$$

· conjugate of z is $z^* = x - jy = r(-\theta) = r e^{-j\theta}$

$$\hookrightarrow z^* = r^2 = x^2 + y^2$$

· addition & subtraction are easier in rectangular form

$$\hookrightarrow z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$\hookrightarrow z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

· multiplication & division are easier in polar form

$$\hookrightarrow z_1 \cdot z_2 = r_1 \angle \theta_1 \cdot r_2 \angle \theta_2 = (r_1 r_2) \angle (\theta_1 + \theta_2)$$

$$\hookrightarrow \frac{z_1}{z_2} = \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \left(\frac{r_1}{r_2}\right) \angle (\theta_1 - \theta_2)$$

PHASORS

· given sinusoid $v(t) = V_m \cos(\omega t + \theta)$, its phasor is complex # $\tilde{V} = V_m e^{j\theta} = V_m \angle \theta$

↳ transformation from sinusoid in time-domain to phasor in complex-domain (aka phasor-domain or frequency-domain)

· phasor rep amp V_m & phase θ but not angular freq ω

↳ every phasor is associated w/specific freq (but not explicitly rep)

↳ when several phasors are manipulated tgt, must be associated w/same freq

· phasors are useful for adding sinusoids w/same freq & solving AC circuits

· relation of $v(t)$ & \tilde{V} is $v(t) = \operatorname{Re}\{\tilde{V} e^{j\omega t}\}$

$$= \operatorname{Re}\{V_m e^{j\theta} e^{j\omega t}\}$$

$$= \operatorname{Re}\{V_m e^{j(\omega t + \theta)}\}$$

$$= V_m \cos(\omega t + \theta)$$


BASIC PHASOR RELATIONS

· for resistor, we have Ohm's law: $v(t) = R i(t)$

$$\hookrightarrow i(t) = I_m \cos(\omega t + \theta_i)$$

$$\hookrightarrow v(t) = R I_m \cos(\omega t + \theta_i)$$

· in phasor-domain:

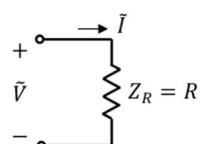

$$\hookrightarrow \tilde{I} = I_m \angle \theta_i$$

$$\hookrightarrow \tilde{V} = V_m \angle \theta_v$$

$$= R I_m \angle \theta_i$$

$$\tilde{V} = R \tilde{I}$$

◦ Ohm's Law

◦ R is a real #

$$\hookrightarrow V_m = R I_m$$


$$\hookrightarrow \theta_v = \theta_i$$

· impedance is $Z = \frac{\tilde{V}}{\tilde{I}}$

↳ for resistance, $Z_R = R$ (i.e. real)

$$\hookrightarrow \tilde{V} = Z_L \tilde{I}$$

· phasor diagram:

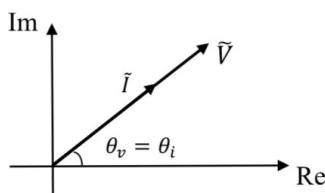

$\hookrightarrow \tilde{V}$ & \tilde{I} are in-phase since $\theta_v = \theta_i$

· for inductors, in time-domain, $v(t) = L \frac{di(t)}{dt}$

$$\hookrightarrow i(t) = I_m \cos(\omega t + \theta_i)$$


$$\hookrightarrow v(t) = L I_m [-\omega \sin(\omega t + \theta_i)]$$

$$\circ \text{since } -\sin \alpha = \cos(\alpha + \frac{\pi}{2}), \quad v(t) = \omega L I_m \cos(\omega t + \theta_i + \frac{\pi}{2})$$

$$\circ \omega L I_m = V_m$$

$$\circ \theta_i + \frac{\pi}{2} = \theta_v$$

in phasor-domain:

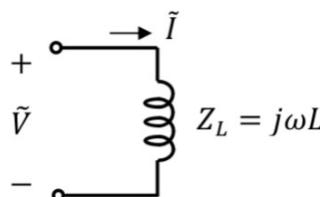

$$\hookrightarrow \tilde{I} = I_m e^{j\theta_i}$$

$$= I_m e^{j\theta_i}$$

$$\hookrightarrow \tilde{V} = V_m e^{j\theta_v}$$

$$= V_m e^{j\theta_v}$$

$$= \omega L I_m e^{j(\theta_i + \frac{\pi}{2})}$$

$$= \omega L (I_m e^{j\theta_i}) e^{j\frac{\pi}{2}}$$


$$\tilde{V} = j\omega L \tilde{I}$$

· impedance of inductance is $Z_L = \frac{\tilde{V}}{\tilde{I}} = j\omega L$

\hookrightarrow purely imaginary & rve

$$\hookrightarrow \tilde{V} = Z_L \tilde{I}$$

· phasor diagram:

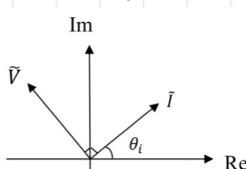

NOTE

$$\cdot j = 1 \angle 90^\circ$$

$$\cdot -j = 1 \angle -90^\circ$$

$$\hookrightarrow V_m = \omega L I_m$$

$$\hookrightarrow \theta_v = \theta_i + \frac{\pi}{2}$$

$$\hookrightarrow \tilde{V} \text{ leads } \tilde{I} \text{ by } \frac{\pi}{2}$$

$$\hookrightarrow \tilde{I} \text{ lags } \tilde{V} \text{ by } \frac{\pi}{2}$$

· for capacitors, in time-domain, $i(t) = C \frac{dv(t)}{dt}$


$$\hookrightarrow v(t) = V_m \cos(\omega t + \theta_v)$$

$$\hookrightarrow i(t) = C V_m [-\omega \sin(\omega t + \theta_v)]$$

$$= \omega C V_m \cos(\omega t + \theta_v + \frac{\pi}{2})$$

- $\omega C V_m = I_m$
- $\theta_v + \frac{\pi}{2} = \theta_i$

in phasor-domain:

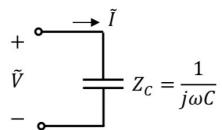


$$\begin{aligned}\hookrightarrow \tilde{I} &= I_m e^{j\theta_i} \\ &= \omega C V_m e^{j(\theta_v + \frac{\pi}{2})} \\ &= j\omega C \tilde{V}\end{aligned}$$

$$\begin{aligned}\hookrightarrow \tilde{V} &= \frac{1}{j\omega C} \tilde{I} \\ \text{impedance of capacitance is } Z_c &= \frac{\tilde{V}}{\tilde{I}} \\ &= \frac{1}{j\omega C} \\ Z_c &= -j \frac{1}{\omega C}\end{aligned}$$

- purely imaginary & -ve
- $\tilde{V} = Z_c \tilde{I}$

phasor diagram:

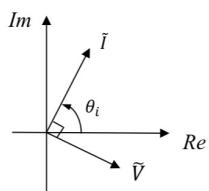

$$\begin{aligned}\hookrightarrow \tilde{V} &= V_m \angle \theta_v \\ &= \frac{1}{j\omega C} \tilde{I} \\ &= -j \frac{1}{\omega C} (I_m \angle \theta_i) \\ &= (\frac{1}{\omega C} I_m) \angle (\theta_i - \frac{\pi}{2}) \\ \bullet V_m &= \frac{1}{\omega C} I_m \\ \bullet \theta_v &= \theta_i - \frac{\pi}{2} \\ \hookrightarrow \tilde{V} &\text{ lags } \tilde{I} \text{ by } \frac{\pi}{2}\end{aligned}$$

Kirchhoff's Laws:

↳ KCL in phasor domain is $\sum_n \tilde{I}_n = 0$


↳ KVL in phasor domain is $\sum_n \tilde{V}_n = 0$

IMPEDANCE AND ADMITTANCE


- for R , L , C , or combo, impedance Z is defined in phasor domain to be $Z = \frac{\tilde{V}}{\tilde{I}}$
- ↳ Z is complex but it's not phasor b/c it's not associated w/sinusoid & also function of ω
- ↳ $Z = R + jX$
 - R is resistance
 - X is reactance
 - all Z , R , & X are measured in Ohms (Ω)
- admittance is defined as $Y = \frac{\tilde{I}}{\tilde{V}} = \frac{1}{Z}$
- ↳ $Y = G + B_j$
 - G is conductance
 - B is susceptance
 - all Y , G , & B are measured in Siemens (S or Ω^{-1})

SERIES AND PARALLEL IMPEDANCES

· series impedances:

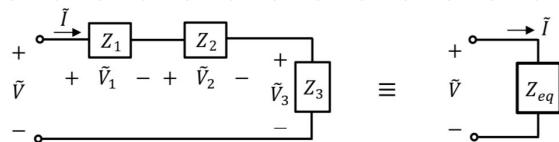

\equiv

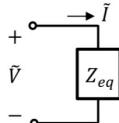

$$\begin{aligned} \hookrightarrow \tilde{V} &= \tilde{V}_1 + \tilde{V}_2 + \tilde{V}_3 \\ &= Z_1 \tilde{I} + Z_2 \tilde{I} + Z_3 \tilde{I} \\ &= (Z_1 + Z_2 + Z_3) \tilde{I} \end{aligned}$$


$$\hookrightarrow \tilde{V} = Z_{eq} \tilde{I}$$

◦ equivalent impedance is $Z_{eq} = Z_1 + Z_2 + Z_3$


$$\hookrightarrow \text{voltage-division relations: } \tilde{V}_i = \frac{Z_i}{Z_1 + Z_2 + Z_3} \tilde{V}$$

◦ $i = 1, 2, 3$

· parallel impedances:

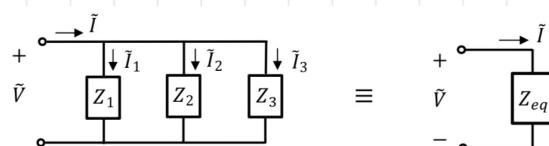

\equiv

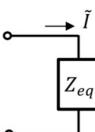

$$\begin{aligned} \hookrightarrow \tilde{I} &= \tilde{I}_1 + \tilde{I}_2 + \tilde{I}_3 \\ &= \frac{\tilde{V}}{Z_1} + \frac{\tilde{V}}{Z_2} + \frac{\tilde{V}}{Z_3} \\ &= \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) \tilde{V} \end{aligned}$$

$$\hookrightarrow \tilde{I} = \frac{\tilde{V}}{Z_{eq}}$$

◦ equivalent impedance is $\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$ or $Y_{eq} = Y_1 + Y_2 + Y_3$

$$\hookrightarrow \text{current-division relations: } \tilde{I}_i = \frac{Y_i}{Y_1 + Y_2 + Y_3} \tilde{I}$$

◦ $i = 1, 2, 3$

· special cases for 2 impedances in parallel:

$$\bullet Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$\bullet \tilde{I}_1 = \frac{Z_2}{Z_1 + Z_2} \tilde{I}$$

$$\bullet \tilde{I}_2 = \frac{Z_1}{Z_1 + Z_2} \tilde{I}$$

AC CIRCUIT ANALYSIS USING PHASORS AND IMPEDANCES

· procedure for AC circuit analysis:

1) convert circuit from time domain into phasor domain

◦ replace all currents & voltages by their phasors

◦ replace all elements by their impedances

2) solve circuit in phasor domain


◦ similar to resistive circuits

3) convert result from phasor to time domain

· e.g. (1) Find $i(t)$, $v_R(t)$, $v_L(t)$, and $v_C(t)$.

(2) Draw phasor diagram.

Note: freq is $\omega = 500$

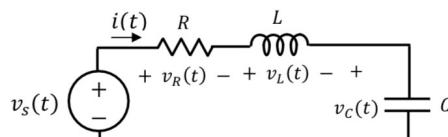

$$R = 10 \Omega$$


$$L = 20 mH$$

$$C = 100 \mu F$$

$$v_s(t) = 20 \cos(500t + 15^\circ) \quad (V)$$

SOLUTION

Phasor-domain circuit:

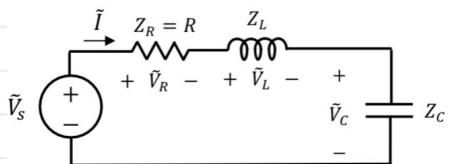

$$\tilde{V}_s = 20 \angle 15^\circ$$

$$\begin{aligned} Z_L &= j\omega L \\ &= j(500)(20 \cdot 10^{-3}) \\ &= j10 \Omega \\ Z_C &= -j \frac{1}{\omega C} \\ &= -j \frac{1}{500(100 \cdot 10^{-6})} \\ &= -j20 \Omega \end{aligned}$$

$$\begin{aligned} \text{KVL: } \tilde{V}_s &= \tilde{V}_R + \tilde{V}_L + \tilde{V}_C \\ &= R\tilde{I} + Z_L\tilde{I} + Z_C\tilde{I} \\ &= (R + Z_L + Z_C)\tilde{I} \\ &= Z_{eq}\tilde{I} \end{aligned}$$

$$\begin{aligned} Z_{eq} &= R + Z_L + Z_C \\ &= 10 + j10 - j20 \\ &= 10 - j10 \\ &= 10(1 - j) \\ &= 10\sqrt{2} \left(\frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}} \right) \\ &= 10\sqrt{2} (\cos(-45^\circ) + j \sin(-45^\circ)) \\ &= 10\sqrt{2} \angle(-45^\circ) \end{aligned}$$

$$\begin{aligned} \tilde{I} &= \frac{\tilde{V}_s}{Z_{eq}} \\ &= \frac{20 \angle 15^\circ}{10\sqrt{2} \angle -45^\circ} \\ &= \sqrt{2} \angle 60^\circ \end{aligned}$$

Convert to time domain:

$$i(t) = \sqrt{2} \cos(500t + 60^\circ) A$$

$$\begin{aligned} \tilde{V}_R &= R\tilde{I} \\ &= 10\sqrt{2} \angle 60^\circ \end{aligned}$$

$$\begin{aligned} \tilde{V}_L &= Z_L\tilde{I} \\ &= (j10)(\sqrt{2} \angle 60^\circ) \\ &= (10 \angle 90^\circ)(\sqrt{2} \angle 60^\circ) \\ &= 10\sqrt{2} \angle 150^\circ \end{aligned}$$


$$v_R(t) = 10\sqrt{2} \cos(500t + 60^\circ) V$$

$$v_L(t) = 10\sqrt{2} \cos(500t + 150^\circ) V$$

$$\begin{aligned} \tilde{V}_C &= Z_C\tilde{I} \\ &= (-j20)(\sqrt{2} \angle 60^\circ) \\ &= (20 \angle -90^\circ)(\sqrt{2} \angle 60^\circ) \\ &= 20\sqrt{2} \angle -30^\circ \end{aligned}$$

$$v_C(t) = 20\sqrt{2} \cos(500t - 30^\circ) V$$

Phasor diagram:

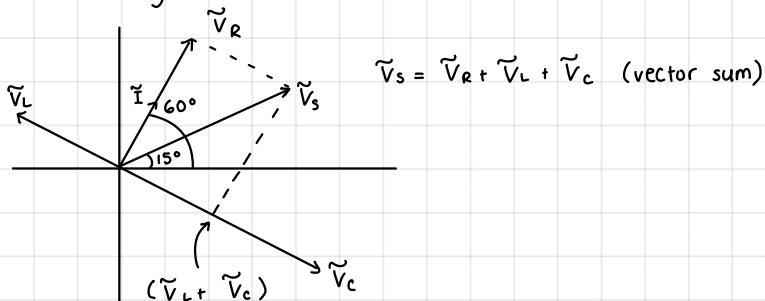

in prev example, if $C = 200 \mu F$, then:

$$\hookrightarrow Z_C = -j \frac{1}{\omega C} = -j10 = -Z_L$$

$$\hookrightarrow Z_C + Z_L = 0$$

$$\hookrightarrow Z_{eq} = R + Z_L + Z_C = 10$$

· combo of inductor & capacitor looks like short circuit

$$\hookrightarrow \tilde{I} = \frac{\tilde{V}_s}{R} = \frac{20 \angle 15^\circ}{10} = 2 \angle 15^\circ$$

$\hookrightarrow \tilde{V}_L + \tilde{V}_C = 0$ but:

- $\tilde{V}_L = j\omega L \tilde{I}$
 $= j10(\sqrt{2} \angle 15^\circ)$

$\neq 0$

- $\tilde{V}_C = -j\frac{1}{\omega C} \tilde{I}$
 $= -j10(2 \angle 15^\circ)$

$\neq 0$

· series resonance happens when $Z_L + Z_C = 0$


$$\hookrightarrow \omega L = \frac{1}{\omega C} \quad \text{or} \quad \omega = \frac{1}{\sqrt{LC}}$$

\hookrightarrow in time domain, $v_L(t) \& v_C(t)$ are sinusoids that are -ve of each other

chapter 9


NODAL ANALYSIS AND MESH ANALYSIS

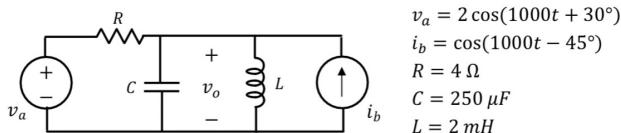- procedures for AC circuits is same as for resistive DC circuits, except they're applied in phasor domain
- e.g. Find $v_o(t)$ in the circuit shown below, using nodal analysis.



SOLUTION

In phasor domain:

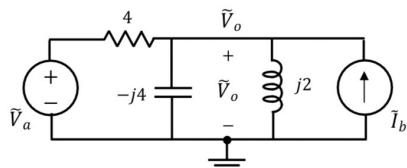

$$\hookrightarrow \tilde{V}_a = 2 \angle 30^\circ$$

$$\hookrightarrow \tilde{I}_b = 1 \angle -45^\circ$$

$$\hookrightarrow Z_R = 4$$

$$\hookrightarrow Z_C = -j \frac{1}{1000(250 \cdot 10^{-6})} = -j4$$

$$\hookrightarrow Z_L = j(1000)(2 \cdot 10^{-3}) = j2$$

KCL:

$$0 = \frac{\tilde{V}_o - \tilde{V}_a}{4} + \frac{\tilde{V}_o}{-j4} + \frac{\tilde{V}_o}{j2} - \tilde{I}_b$$

$$0 = j(\tilde{V}_o - \tilde{V}_a) - \tilde{V}_o + 2\tilde{V}_o - (j4)\tilde{I}_b$$

$$0 = j\tilde{V}_o - \tilde{V}_o + 2\tilde{V}_o - j\tilde{V}_a - (j4)\tilde{I}_b$$

$$0 = \tilde{V}_o(j+1) - j\tilde{V}_a - j4\tilde{I}_b$$

$$\tilde{V}_o(j+1) = j\tilde{V}_a + j4\tilde{I}_b$$

$$\tilde{V}_o(j+1) = (1 \angle 90^\circ)(2 \angle 30^\circ) + (4 \angle 90^\circ)(1 \angle -45^\circ)$$

$$\tilde{V}_o(\sqrt{2} \angle 45^\circ) = 2 \angle 120^\circ + 4 \angle 45^\circ$$

$$\tilde{V}_o(\sqrt{2} \angle 45^\circ) = (-1 + j\sqrt{3}) + (2\sqrt{2} + j2\sqrt{2})$$

$$\tilde{V}_o(\sqrt{2} \angle 45^\circ) \approx 1.82843 + j4.56048$$

$$\tilde{V}_o \approx \frac{4.91336 \angle 68.1527^\circ}{\sqrt{2} \angle 45^\circ}$$

$$\approx 3.47427 \angle 23.1527^\circ$$

$$\approx 3.47 \angle 23.15^\circ$$

$$v_o(t) = 3.47 \cos(1000t + 23.15^\circ)$$

$\rightarrow j+1 :$

$$r = \sqrt{1^2 + 1^2}$$

$$\theta = \tan^{-1}\left(\frac{1}{1}\right)$$


$$= \sqrt{2}$$

$$= 45^\circ$$

LINEARITY AND SUPERPOSITION

- when circuit has independent sources w/ diff freq., superposition must be used
- apply superposition in time domain, solve each individual circuit in phasor domain, & add individual responses in time domain


- e.g. Find $v_o(t)$.

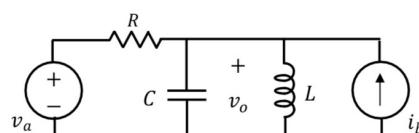

$v_a = 2 \cos(1000t + 30^\circ)$
 $i_b = \cos(2000t - 45^\circ)$
 $R = 4 \Omega$
 $C = 250 \mu F$
 $L = 2 mH$

SOLUTION

For v_a alone, $\omega_1 = 1000$:

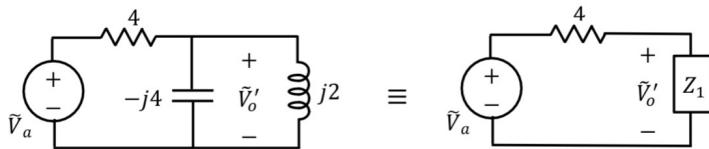

$$\tilde{V}_a = 2 \angle 30^\circ$$


$$Z_L = j\omega L = j(1000)(2 \cdot 10^{-3}) \\ = j2 \\ Z_C = -j \frac{1}{\omega C} = -j \left(\frac{1}{1000 \cdot 250 \cdot 10^{-6}} \right) \\ = -j4$$

$$Z_T = \frac{Z_L \parallel Z_C}{(j2)(-j4)} \\ = \frac{j2 \cdot -j4}{8} \\ = \frac{-j2}{-j} \\ = j4$$

$$\text{Using voltage division: } \tilde{V}_{o1} = \tilde{V}_a \left(\frac{z_1}{4+z_1} \right) \\ = (2 \angle 30^\circ) \left(\frac{j4}{4+j4} \right) \\ = (2 \angle 30^\circ) \left(\frac{4 \angle 90^\circ}{4\sqrt{2} \angle 45^\circ} \right) \\ = (2 \angle 30^\circ) \left(\frac{\sqrt{2}}{2} \angle 45^\circ \right) \\ = \sqrt{2} \angle 75^\circ$$

$$v_{o1}(t) = \sqrt{2} \cos(1000t + 75^\circ)$$

For i_b alone, $\omega_2 = 2000$:

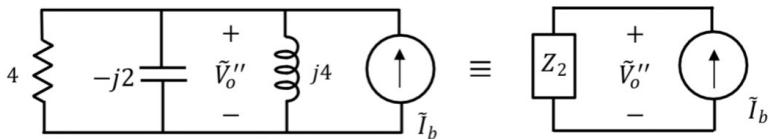

$$\tilde{I}_b = 1 \angle (-45^\circ)$$

$$Z_L = j\omega L = j(2000)(2 \cdot 10^{-3}) \\ = j4 \\ Z_C = -j \frac{1}{\omega C} = -j \frac{1}{2000 \cdot 250 \cdot 10^{-6}}$$

$$\frac{1}{Z_T} = \frac{1}{4} + \frac{1}{Z_L} + \frac{1}{Z_C} \\ = \frac{1}{4} + \frac{1}{j4} + \frac{1}{-j2} \\ = \frac{1}{4} + j(-\frac{1}{4} + \frac{1}{2}) \\ = \frac{1}{4} + j\frac{1}{4} \\ = \frac{\sqrt{2}}{4} \angle 45^\circ$$

$$Z_2 = 2\sqrt{2} (\angle -45^\circ)$$

$$\tilde{V}_{o2} = Z_2 \tilde{I}_b \\ = (2\sqrt{2} (\angle -45^\circ))(1 \angle (-45^\circ)) \\ = 2\sqrt{2} (\angle -90^\circ)$$

$$v_{o2}(t) = 2\sqrt{2} \cos(2000t - 90^\circ)$$

Using superposition in time domain, $v_o(t) = \sqrt{2} \cos(1000t + 75^\circ) + 2\sqrt{2} \cos(2000t - 90^\circ)$.


superposition can be applied in phasor domain if all sources have same freq

parallel resonance: parallel connection of inductor & capacitor has impedance

$$Z = \frac{j\omega L \cdot j\frac{1}{\omega C}}{j\omega L - j\frac{1}{\omega C}} = \frac{\omega L}{\omega L - \frac{1}{\omega C}}$$

↳ magnitude is $|Z| = \sqrt{\omega^2 LC - \frac{1}{\omega^2}}$


↳ plotting $|Z|$ as function of ω :

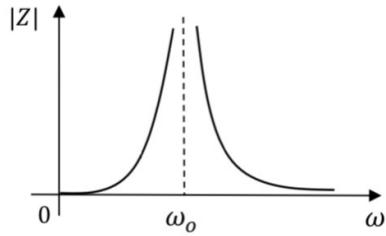

• $|Z| \rightarrow \infty$ (i.e. open circuit) when $\omega_0 L - \frac{1}{\omega_0 C} = 0$ or $\omega_0 = \sqrt{\frac{1}{LC}}$ (resonance freq)

SOURCE TRANSFORMATION

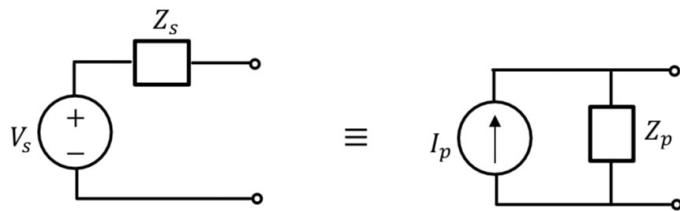• source transformation can be applied in phasor domain when all sources have same freq




$$V_s = Z_p I_p$$

$$I_p = \frac{V_s}{Z_s}$$

$$Z_s = Z_p$$


THEVENIN AND NORTON EQUIVALENT CIRCUITS

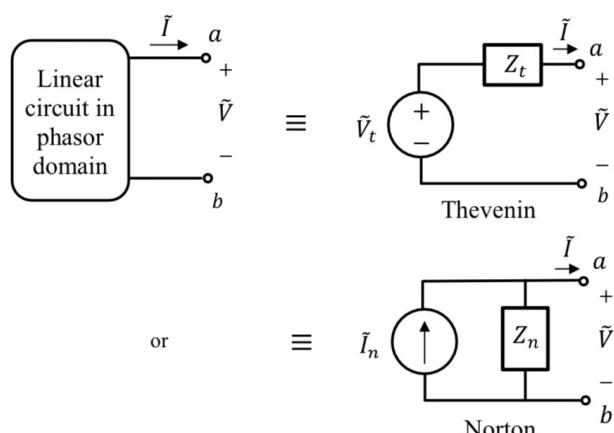• to apply Thevenin & Norton theorems to AC circuits in phasor domain, sources must have same freq



- ↳ $\tilde{V}_t = \tilde{V}_{oc}$
- ↳ $I_n = \tilde{I}_{sc}$
- ↳ $Z_t = Z_n = \frac{\tilde{V}_{oc}}{\tilde{I}_{sc}}$
- ↳ $Z_t = Z_n = Z_{eq}$
 - equivalent impedance
- ↳ $Z_t = Z_n = \frac{\tilde{V}_s}{\tilde{I}_s}$
 - external source
 - use when circuit has only dependent source

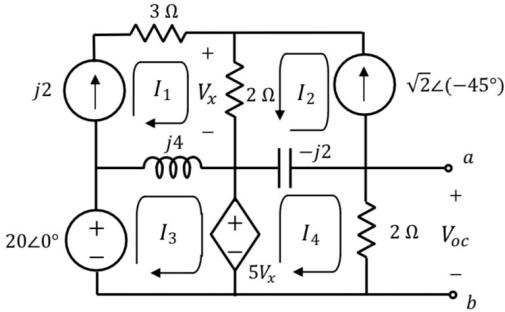e.g Find Thevenin equivalent circuit between a and b ?



SOLUTION

Use mesh analysis to find V_{oc} :

$$I_1 = j2 = 2 \angle 90^\circ$$

$$I_2 = \sqrt{2} \angle (-45^\circ) = 1-j$$

$$V_x = 2(I_1 + I_2)$$

$$= 2(j2 + 1-j)$$

$$= 2(1+j)$$

$$= 2 + j2$$

$$= 2\sqrt{2} \angle 45^\circ$$

KVL around I_3 :

$$0 = -20 + j4(I_3 - I_1) + 5V_x$$

$$0 = -20 + j4I_3 - j4I_1 + 5V_x$$

$$j4I_3 = 20 + j4I_1 - 5V_x$$

$$j4I_3 = 20 + j4(j2) - 5(2 + j2)$$

$$j4I_3 = 20 - 8 - 10 - j10$$

$$j4I_3 = 2 - j10$$

$$I_3 = \frac{2 - j10}{j4} \approx \frac{2\sqrt{26}}{1} \angle -78.69^\circ$$

$$\approx 2\sqrt{26} \angle -168.69^\circ$$


$$V_{oc} = 2I_4$$

$$= 2(j6)$$

$$= j12$$

$$V_t = j12$$

Find I_{sc} :

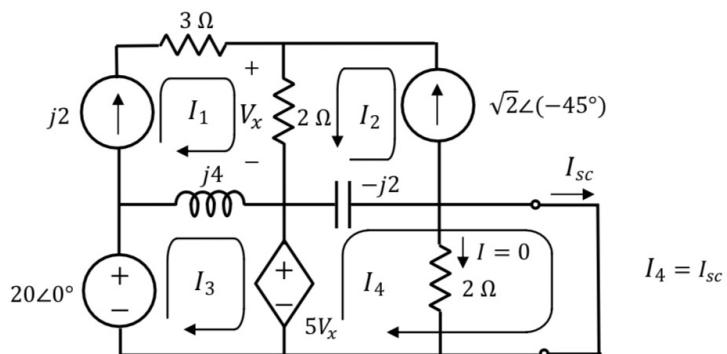

$\hookrightarrow I_1, I_2, I_3, V_x$ are same as before

KVL around I_4 :

$$0 = -5V_x + (-j2)(I_4 + I_2)$$

$$0 = -5V_x - j2I_4 - j2I_2$$


$$j2I_4 = -5V_x - j2I_2$$

$$j2I_4 = -5(2 + j2) - j2(1-j)$$

$$j2I_4 = -10 - j10 - j2 - 2$$

$$\begin{aligned}
 jZI_4 &= -12 - j12 \\
 I_4 &= \frac{12\sqrt{2} \angle 225^\circ}{2 \angle 90^\circ} \\
 &= 6\sqrt{2} \angle 135^\circ \\
 Z_t &= \frac{V_{oc}}{I_{sc}} \\
 &= \frac{12 \angle 90^\circ}{6\sqrt{2} \angle 135^\circ} \\
 &= \sqrt{2} (\angle -45^\circ) \\
 &= 1 - j \quad \rightarrow \text{capacitive since imaginary part is -ve}
 \end{aligned}$$

Thevenin equivalent circuit:

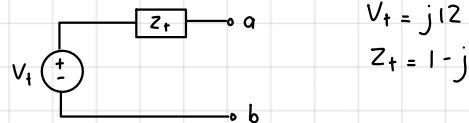


NOTE

if circuit has sources w/diff freq, then each source has Thevenin/Norton equivalent that are entirely diff since their freq are diff
• can't combine circuits

AC OP-AMP CIRCUITS

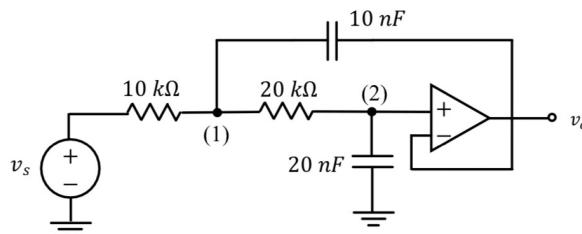e.g. Given $v_s = 12 \cos(5000t)$, find v_o assuming ideal op-amp.



SOLUTION

$$\begin{aligned}
 C_1 &= 10 \text{ nF} = -j \frac{1}{\omega C_1} \\
 &= -j \frac{1}{5000(20 \cdot 10^{-9})} \\
 &= -j 10 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 C_2 &= 20 \text{ nF} = -j \frac{1}{\omega C_2} \\
 &= -j \frac{1}{5000(20 \cdot 10^{-9})} \\
 &= -j 10 \text{ k}\Omega
 \end{aligned}$$

Phasor domain:

$$V_s = 12 \angle 0^\circ = 12$$

$$V_2 = V_o$$

$$\begin{aligned}
 0 &= \frac{V_1 - V_s}{10} + \frac{V_1 - V_2}{20} + \frac{V_1 - V_o}{-j20} \\
 0 &= \frac{V_1}{10} - \frac{V_s}{10} + \frac{V_1}{20} - \frac{V_o}{20} + \frac{V_1}{-j20} + \frac{V_o}{j20} \\
 0 &= V_1 \left(\frac{3}{20} + \frac{j}{20} \right) - \frac{V_s}{10} + V_o \left(-\frac{1}{20} - \frac{j}{20} \right) \\
 \frac{V_s}{10} &= \frac{V_1}{20} (3 + j) + \frac{V_o}{20} (-1 - j)
 \end{aligned}$$

$$2V_s = V_1(3 + j) - V_o(1 + j) \quad (1)$$

Sub (2) into (1).

$$2V_s = V_o(1 + j2)(3 + j) - V_o(1 + j)$$

$$2V_s = V_o(3 + j + j6 + j^2 2) - V_o(1 + j)$$

$$2V_s = V_o(1 + j7) - V_o(1 + j)$$

$$2V_s = V_o(1 + j7 - 1 - j)$$

$$24 \angle 0^\circ = V_o(j6)$$

$$V_o = \frac{24 \angle 0^\circ}{6 \angle 90^\circ}$$

$$V_o = 4 \angle -90^\circ$$

$$\begin{aligned}
 0 &= \frac{V_2 - V_1}{20} + \frac{V_2}{j10} \\
 0 &= \frac{V_o}{20} - \frac{V_1}{20} + \frac{V_o}{j10} \\
 V_1 &= V_o(1 + j2) \quad (2)
 \end{aligned}$$

Time domain: $v_o = 4 \cos(5000t - 90^\circ) = 4 \sin(5000t)$

chapter 10

AVERAGE POWER AND RMS VALUE

- when applying periodic voltage $v(t)$ w/ period T to resistor R :

↳ instantaneous absorbed power is $p(t) = v(t)i(t) = \frac{v^2(t)}{R}$

↳ avg power is $P_{av} = \frac{1}{T} \int_0^T p(t) dt$

- Root-Mean-Square (rms) value of $v(t)$ is $V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$

↳ constant value

- avg power is $P_{av} = \frac{V_{rms}^2}{R}$, which is also a constant

- RMS value V_{rms} is aka effective value V_{eff} since $P_{av} = \frac{V_{rms}^2}{R}$ is similar to DC power $P = \frac{V_{dc}^2}{R}$ w/ $V_{dc} = V_{rms}$

- periodic current $i(t)$ w/ period T has RMS value $I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$

↳ $P_{av} = R I_{rms}^2$

NOTE

$v(t)$ is periodic
but not necessarily
a sinusoid

- to determine RMS value for sinusoid:

↳ $v(t) = V_m \cos(\omega t + \theta)$

$$\begin{aligned} \text{↳ } V_{rms} &= \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t + \theta) dt} \\ &= \left(\frac{V_m^2}{T} \int_0^T \frac{1 + \cos(2\omega t + 2\theta)}{2} dt \right)^{1/2} \\ &= \left(\frac{V_m^2}{2T} \left[t + \frac{1}{2\omega} \sin(2\omega t + 2\theta) \right]_0^T \right)^{1/2} \\ &= \left(\frac{V_m^2}{2T} \left(T + \frac{1}{2\omega} \sin(2\omega T + 2\theta) - \frac{1}{2\omega} \sin(2\theta) \right) \right)^{1/2} \end{aligned}$$

Since $T = \frac{2\pi}{\omega} \rightarrow 2\pi = \omega T$


$$\begin{aligned} V_{rms} &= \left(\frac{V_m^2}{2T} \left(T + \frac{1}{2\omega} \sin(4\pi + 2\theta) - \frac{1}{2\omega} \sin(2\theta) \right) \right)^{1/2} \\ &= \left(\frac{V_m^2}{2T} \left(T + \frac{1}{2\omega} \sin(2\theta) - \frac{1}{2\omega} \sin(2\theta) \right) \right)^{1/2} \\ &= \left(\frac{V_m^2}{2T} \cdot T \right)^{1/2} \\ &= \sqrt{\frac{V_m^2}{2}} \\ &= \frac{V_m}{\sqrt{2}} \end{aligned}$$

↳ $V_{rms} = \frac{V_m}{\sqrt{2}}$ for sinusoid

- current $i(t) = I_m \cos(\omega t + \theta)$ has RMS value $I_{rms} = \frac{I_m}{\sqrt{2}}$

- for triangular voltage, $V_{rms} = \frac{V_m}{\sqrt{3}}$

↳

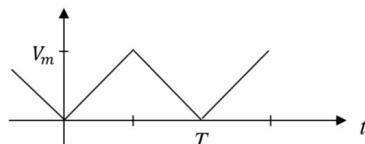

- let $v(t) = V_{m1} \cos(\omega_1 t + \theta_1) + V_{m2} \cos(\omega_2 t + \theta_2)$ w/ $V_{rms1} = \frac{V_{m1}}{\sqrt{2}}$ { $V_{rms2} = \frac{V_{m2}}{\sqrt{2}}$

↳ to find RMS value for sum of sinusoids:

◦ if $\omega_1 \neq \omega_2$, $V_{rms} = \sqrt{V_{rms1}^2 + V_{rms2}^2}$

◦ if $\omega_1 = \omega_2$, $V_{rms} = \sqrt{\frac{1}{2} V_{m1}^2 + \frac{1}{2} V_{m2}^2 + V_{m1} V_{m2} \cos(\theta_1 - \theta_2)}$ (combine into 1 sinusoid in phasor domain first)

- RMS value of V_{dc} isn't $\frac{V_{dc}}{\sqrt{2}}$


↳ $V_{rms} = V_{dc}$

MAXIMUM AVERAGE POWER TRANSFER

- load Z_L is connected to given AC linear circuit ? find Z_L st it absorbs max avg power

↳ replace circuit w/ Thevenin equivalent \tilde{V}_{th} { $Z_{th} = R_{th} + jX_{th}$

5

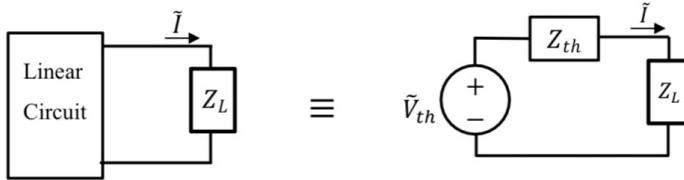

case 1: load is complex impedance $Z_L = R_L + jX_L$

↳ max avg power is absorbed when $R_L = R_{th}$ & $X_L = -X_{th}$

$$\circ Z_L = Z_{th}^*$$

↳ if Z_{th} is capacitive, then Z_L is inductive & vice versa

$$\hookrightarrow P_{max} = \frac{|V_{th}|^2}{8R_{th}} = \frac{V_{rms}^2}{4R_{th}}$$

case 2: load is real

↳ i.e. $Z_L = R_L$

$$\hookrightarrow R_L = |Z_{th}| = \sqrt{R_{th}^2 + X_{th}^2}$$

$$\hookrightarrow P_{max} = \frac{1}{2} |\tilde{I}|^2 R_L = I_{rms}^2 R_L$$

ACTIVE POWER, REACTIVE POWER, AND POWER FACTOR

for general element w/ $T = \frac{2\pi}{\omega}$ as time period.

$$\hookrightarrow v(t) = V_m \cos(\omega t + \theta_v)$$

$$\hookrightarrow i(t) = I_m \cos(\omega t + \theta_i)$$

take $i(t)$ as time-ref, subtract θ_i from both to give:

$$\hookrightarrow v(t) = V_m \cos(\omega t + \theta_v - \theta_i)$$

$$\hookrightarrow i(t) = I_m \cos(\omega t)$$

instantaneous power is $p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos(\omega t)$

$$\hookrightarrow \text{using trig identities, } p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \cos(2\omega t) - \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \sin(2\omega t)$$

active(real) power is $P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$

$$\hookrightarrow V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\hookrightarrow I_{rms} = \frac{I_m}{\sqrt{2}}$$

↳ P is constant

↳ rep portion of power that's transformed from electric to non-electric energy (e.g. heat)

reactive power is $Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$

↳ Q is constant

↳ rep portion of power that's not transformed into non-electric energy but exchanged btwn circuit elements

rewrite $p(t)$ using P & Q : $p(t) = P + P \cos(2\omega t) - Q \sin(2\omega t)$

$$\hookrightarrow \text{avg power is } P_{av} = \frac{1}{T} \int_0^T p(t) dt \quad \text{where } T = \text{period}$$

↳ integral of P is P

↳ integrals of last 2 terms are 0 since integration is over complete period

↳ average power $P_{av} = \text{active/real power } P$

↳ i.e. $P_{av} = P$

power factor is $\text{pf} = \cos(\theta_v - \theta_i)$

$$\hookrightarrow P = V_{rms} I_{rms} \cdot \text{pf}$$

↳ since $0 \leq \text{pf} \leq 1$, power factor rep percentage of product $V_{rms} I_{rms}$ that's real/active power

↳ pf depends only on angles


for power for resistor, $\theta_v = \theta_i$ & $\text{pf} = \cos 0 = 1$

$$\hookrightarrow P = \frac{1}{2} V_m I_m = V_{rms} I_{rms}$$

$$\hookrightarrow \text{since } V_m = R I_m \text{ & } V_{rms} = R I_{rms}, \quad P = \frac{1}{2} R I_m^2 = R I_{rms}^2 = \frac{1}{2} \frac{V_m^2}{R} = \frac{V_{rms}^2}{R}$$

- ↳ since $\sin 0 = 0$, reactive power is $Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = 0$
 - $Q = 0$ for resistors always
- for power for inductor, $\theta_v - \theta_i = 90^\circ \nparallel \text{pf} = \cos 90^\circ = 0$
 - ↳ $P = 0$
 - ↳ since $\sin(\theta_v - \theta_i) = \sin 90^\circ = 1$, then $Q = \frac{1}{2} V_m I_m = V_{rms} I_{rms}$
 - always +ve
 - ↳ since $\tilde{V} = j\omega L \tilde{I}$, $V_m = \omega L I_m$, $\nparallel V_{rms} = \omega L I_{rms}$, $Q = \frac{1}{2} \omega L I_m^2 = \omega L I_{rms}^2 = \frac{1}{2} \frac{V_m^2}{\omega L} = \frac{V_{rms}^2}{\omega L}$
 - ↳ inductor stores energy in 1 half cycle & releases it in other half
- for power for capacitor, $\theta_v - \theta_i = -90^\circ \nparallel \text{pf} = \cos(-90^\circ) = 0$
 - ↳ $P = 0$
 - ↳ since $\sin(\theta_v - \theta_i) = \sin(-90^\circ) = -1$, then $Q = -\frac{1}{2} V_m I_m = -V_{rms} I_{rms}$
 - always -ve
 - ↳ since $\tilde{V} = -j\frac{1}{\omega C} \tilde{I}$, $V_m = \frac{1}{\omega C} I_m$, $\nparallel V_{rms} = \frac{1}{\omega C} I_{rms}$, $Q = -\frac{1}{2} \frac{I_m^2}{\omega C} = -\frac{I_{rms}^2}{\omega C} = -\frac{1}{2} \omega C V_m^2 = -\omega C V_{rms}^2$
 - ↳ conductor doesn't dissipate P & only exchanges Q w/ other circuit elements

COMPLEX POWER AND APPARENT POWER

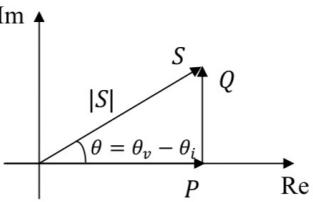- complex power for general element is $S = \frac{1}{2} \tilde{V} \tilde{I}^*$ = $\tilde{V}_{rms} \tilde{I}_{rms}^*$
 - ↳ $\tilde{V}_{rms} = V_{rms} \angle \theta_v$ & $\tilde{I}_{rms} = I_{rms} \angle \theta_i$ are RMS phasors
 - same as regular phasors except for scalar division of magnitudes of $\sqrt{2}$
 - $\tilde{V}_{rms} = \frac{\tilde{V}}{\sqrt{2}}$
 - $\tilde{I}_{rms} = \frac{\tilde{I}}{\sqrt{2}}$
- complex power can be related to active & reactive power
 - ↳ $S = \tilde{V}_{rms} \tilde{I}_{rms}^*$
 - = $(V_{rms} e^{j\theta_v})(I_{rms} e^{-j\theta_i})$
 - = $V_{rms} I_{rms} e^{j(\theta_v - \theta_i)}$
 - = $V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$
 - $S = P + jQ$
- apparent power is $P_{app} = V_{rms} I_{rms}$
 - ↳ $P_{app} = |S| = \sqrt{P^2 + Q^2}$
- convention for units of power:
 - ↳ active P : watt (W)
 - ↳ reactive Q : volt-ampere-reactive (VAR)
 - ↳ complex S : volt-ampere (VA)
 - ↳ apparent $|S|$: volt-ampere (VA)
- power triangle used to compute all kinds of power
 - ↳ 

- ↳ angle of S is $\theta = \theta_v - \theta_i$
- ↳ $\frac{Q}{P} = \frac{\sin(\theta_v - \theta_i)}{\cos(\theta_v - \theta_i)}$
- ↳ $\frac{Q}{P} = \tan(\theta_v - \theta_i)$
- $\theta_v - \theta_i = \tan^{-1}(\frac{Q}{P}) = \cos^{-1}(\text{pf})$

- convention for pf:
 - ↳ pf lagging means \tilde{I} lags \tilde{V}
 - Q +ve (i.e. inductive)

NOTE

- pf leading means $\theta_v - \theta_i$ is -ve
- pf lagging means $\theta_v - \theta_i$ is +ve

↳ pf leading means \tilde{I} leads \tilde{V}

• Q -ve (i.e. capacitive)

· in power calc for impedance, complex power is $S = \tilde{V}_{rms} \tilde{I}^*_{rms}$ & impedance is $Z = R + jX$

$$\hookrightarrow V_{rms} = Z I_{rms}$$

$$\hookrightarrow S = Z \tilde{I}_{rms} \tilde{I}^*_{rms}$$

$$= (R + jX) I^2_{rms}$$


$$= RI^2_{rms} + jX I^2_{rms}$$

$$S = P + jQ$$


$$\bullet P = RI^2_{rms}$$
 (tve for $R \geq 0$)

$$\bullet Q = X I^2_{rms}$$
 (tve for inductive Z & -ve for capacitive Z)

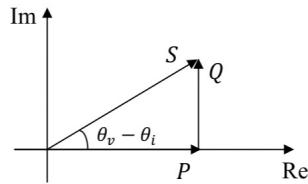· power triangles for impedance $Z = R + jX$:




(Inductive Z)

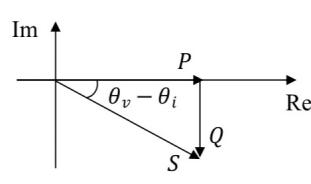

(Capacitive Z)

$$\hookrightarrow \tan(\theta_v - \theta_i) = \frac{Q}{P} = \frac{X}{R}$$

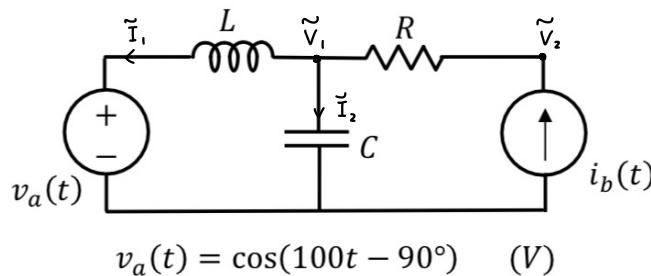· e.g. Find the active and reactive power for every element.



$$R = 1 \Omega$$

$$L = \frac{1}{100} H$$

$$C = \frac{1}{50} F$$

$$i_b(t) = \sqrt{2} \cos(100t + 45^\circ) \quad (\text{A})$$

SOLUTION

In phasor domain:

$$\tilde{V}_a = 1 \angle -90^\circ = -j$$

$$\tilde{I}_b = \sqrt{2} \angle 45^\circ = 1 + j$$

$$Z_L = j\omega L = j(100)(\frac{1}{100}) = j$$

$$Z_C = -j\frac{1}{\omega C} = -j\frac{1}{100(1/50)} = -j\frac{1}{2}$$

Compute currents & voltages using nodal analysis:

$$0 = \frac{\tilde{V}_1 - \tilde{V}_a}{Z_L} + \frac{\tilde{V}_1}{Z_C} - \tilde{I}_b$$

$$\tilde{I}_b = \frac{\tilde{V}_1 + j}{j} + \frac{\tilde{V}_1}{2j}$$

$$1 + j = -j \tilde{V}_1 + 1 + 2j \tilde{V}_1$$

$$j = j \tilde{V}_1$$

$$\tilde{V}_1 = 1 = 1 \angle 0^\circ$$

$$\begin{aligned} \tilde{I}_1 &= \frac{\tilde{V}_1 - \tilde{V}_a}{j} \\ &= \frac{1 - (-j)}{j} \\ &= -j + 1 \end{aligned}$$

$$\tilde{I}_1 = 1 - j = \sqrt{2} \angle -45^\circ$$

$$\begin{aligned} \tilde{I}_2 &= \frac{\tilde{V}_1}{Z_C} \\ &= \frac{1}{2j} \end{aligned}$$

$$\tilde{I}_2 = 2j = 2 \angle 90^\circ$$

$$\begin{aligned} \tilde{I}_b &= \frac{\tilde{V}_2 - \tilde{V}_1}{R} \\ &= \frac{1 - 1}{1} \end{aligned}$$

$$1 + j = \sqrt{5} \angle 26.565^\circ$$

Absorbed power for \tilde{V}_a (PSC):

$$\begin{aligned}
 P_a &= V_{rms} I_{rms} \cos(\theta_v - \theta_i) \\
 &= \left(\frac{1}{\sqrt{2}}\right) \left(\frac{\sqrt{2}}{\sqrt{2}}\right) \cos(-90^\circ - (-45^\circ)) \\
 &= \frac{1}{\sqrt{2}} \cos(-45^\circ) \\
 P_a &= \frac{1}{2} W \quad (\text{actually absorbed}) \\
 Q_a &= V_{rms} I_{rms} \sin(\theta_v - \theta_i) \\
 &= \frac{1}{\sqrt{2}} \sin(-45^\circ) \\
 Q_a &= -\frac{1}{2} \text{ VAR} \quad (\text{capacitive reactive power})
 \end{aligned}$$

Supplied power for \tilde{I}_b (not PSC):

$$\begin{aligned}
 S_b &= \tilde{V}_{2rms} \tilde{I}^*_{brms} \\
 P_b + jQ_b &= \left(\frac{\sqrt{5}}{\sqrt{2}} \angle 26.565^\circ\right) \left(\frac{\sqrt{2}}{\sqrt{2}} \angle -45^\circ\right) \\
 &= \frac{\sqrt{5}}{\sqrt{2}} \angle -18.435^\circ \\
 &= \frac{3}{2} - j\frac{1}{2} \\
 P_b &= \frac{3}{2} W \quad (\text{acc supplied}) \\
 Q_b &= -\frac{1}{2} \text{ VAR} \quad (\text{capacitive reactive power})
 \end{aligned}$$

Power for R:

$$\begin{aligned}
 P_R &= V_{rms} I_{brms} \\
 &= RI^2_{rms} \\
 &= 1 \left(\frac{\sqrt{2}}{\sqrt{2}}\right)^2 \\
 &= 1
 \end{aligned}$$

$$P_R = 1 W$$

$$Q_R = 0$$

Power for L:

$$P_L = 0$$

$$\tilde{V}_L = \tilde{V}_1 - \tilde{V}_a$$

$$= 1 - (-j)$$

$$\tilde{V}_L = 1 + j = \sqrt{2} \angle 45^\circ$$

$$Q_L = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

$$= \frac{\sqrt{2}}{\sqrt{2}} \left(\frac{\sqrt{2}}{\sqrt{2}}\right) \sin(45^\circ + 45^\circ)$$

$$Q_L = 1 \text{ VAR}$$

Power for C:

$$P_C = 0$$

$$\begin{aligned}
 Q_C &= V_{rms} I_{rms} \sin(\theta_v - \theta_i) \\
 &= \left(\frac{1}{\sqrt{2}}\right) \left(\frac{2}{\sqrt{2}}\right) \sin(0^\circ - 90^\circ)
 \end{aligned}$$

$$Q_C = -1 \text{ VAR}$$


NOTE

$$\begin{aligned}
 P_a \text{ \& } Q_a \text{ can also be computed} \\
 \text{from } S_a = \tilde{V}_{rms} \tilde{I}^*_{rms} = P_a + jQ_a \\
 \hookrightarrow S_a = \frac{1}{\sqrt{2}} \angle -90^\circ \cdot \frac{\sqrt{2}}{\sqrt{2}} \angle 45^\circ \\
 &= \frac{1}{\sqrt{2}} \angle -45^\circ \\
 &= \frac{1}{2} - j\frac{1}{2}
 \end{aligned}$$

conservation of power applies to P, Q, & S

$$\hookrightarrow \sum P = 0, \sum Q = 0, \text{ \& } \sum S = 0$$

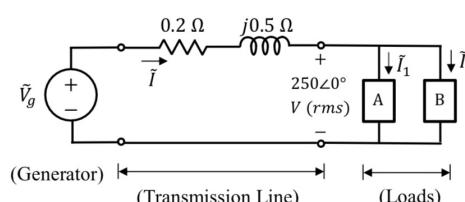- e.g. Two loads A and B are connected to a generator through a transmission line as shown. The voltage at the loads must be maintained at 250 V(rms).



NOTE

simpler methods:

$$\begin{aligned}
 \hookrightarrow Q_C &= -\frac{1}{\omega C} I_{rms}^2 \\
 &= -\frac{1}{100 \left(\frac{1}{50}\right)} \left(\frac{2}{\sqrt{2}}\right)^2 \\
 &= -1 \text{ VAR}
 \end{aligned}$$

$$\begin{aligned}
 \hookrightarrow Q_C &= -\omega C V_{rms}^2 \\
 &= -1 \text{ VAR}
 \end{aligned}$$

- Load A absorbs 8 kW at $p_f_1 = 0.8$ leading.

- Load B absorbs 20 kVA at $p_f_2 = 0.6$ lagging.

SOLUTION

a) Computing pf for combined 2 loads:

Load A :

$$P_A = 8 \text{ kW}$$

$$pf_1 = \cos(\theta_v - \theta_i) = 0.8$$

$$\theta_v - \theta_i = -36.87^\circ \text{ (-ve since pf is leading)}$$

$$\frac{Q_A}{P_A} = \tan(\theta_v - \theta_i)$$

$$Q_A = 8k \tan(-36.87^\circ)$$

$$= -6k \text{ VAR}$$

$$S_A = 8 - j6 \text{ kVA}$$

Load B :

$$P_{app} = |S_B| = V_{rms} I_{rms} = 20 \text{ kVA}$$

$$\theta_v - \theta_i = \cos^{-1}(pf_2) = 53.13^\circ \text{ (+ve since pf_2 is lagging)}$$

$$P_B = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$Q_B = |S_B| \sin(\theta_v - \theta_i)$$

$$= |S_B| pf_2$$

$$= 20k \sin 53.13^\circ$$

$$= 12 \text{ kW}$$

$$= 16k \text{ VAR}$$

$$S_B = 12 + j16 \text{ kVA}$$

$$S_{AB} = S_A + S_B$$

$$pf = \cos 26.565^\circ$$

$$= 8 - j6 + 12 + j16$$

$$pf = 0.894 \text{ (lagging)}$$

$$= 20 + j10$$

$$= 10\sqrt{5} \angle 26.565^\circ \text{ kVA}$$

b) Avg power loss due to transmission line:

$$S = \tilde{V}_{rms} \tilde{I}_{rms}$$

$$\tilde{I}_{rms} = \frac{S}{\tilde{V}_{rms}}$$

$$= \frac{20 + j10}{250}$$

$$= 0.08 + j0.04 \text{ kA}$$

$$I_{rms} = 80 - j40 \text{ A}$$

$$= 40\sqrt{5} \angle -26.565^\circ \text{ A}$$

$$P_{line} = R |\tilde{I}_{rms}|^2$$

$$= 0.2(40\sqrt{5})^2$$

$$= 1600 \text{ W}$$

$$P_{line} = 1.6 \text{ kW} \text{ (power lost)}$$

c) Generated active & reactive powers for source:

$$Q_{line} = X |\tilde{I}_{rms}|^2$$

$$= 0.5(40\sqrt{5})^2$$

$$= 4000 \text{ VAR}$$

$$= 4 \text{ kVAR}$$

$$S_g = 21.6 + j14 \text{ kVA}$$

$$= 25.74 \angle 32.95^\circ \text{ kVA}$$

d) Generator voltage \tilde{V}_g :

$$S_g = \tilde{V}_{grms} \tilde{I}_{grms}$$

$$\tilde{V}_{grms} = \frac{25.74 \angle 32.95^\circ}{40\sqrt{5} \angle 26.565^\circ}$$

$$= 0.286214 \angle 6.385^\circ \text{ kV}$$

$$= 286.214 \angle 6.385^\circ \text{ V}$$

NOTE

only consider power loss from resistance
since inductor just exchanges energy w/
other circuit elements